

Key Note

at

25th Iranian Conference on Electrical Engineering (ICEE 2017)
Tehran, Iran, May 2017

**Currents' Physical Components (CPC) – based power theory
of electrical systems
with nonsinusoidal and asymmetrical voltages and currents: –
– present state and the future**

Leszek S. Czarnecki, IEEE Life Fellow

Titled Professor of Technological Sciences of Poland
Distinguished Professor at School of Electrical Engineering
Louisiana State University, USA

Internet Page: www.lsczar.info

مؤلفه های فیزیکی جریان
تئوری پایه قدرت سیستم های الکتریکی با
جریان ها و ولتاژهای نامتقارن و غیر سینوسی:
شرایط کنونی و آینده

پروفسور لچک چارنسکی

Cost of the electric energy delivery
is related to a main degree to the load apparent power S
which is a product
of RMS values of the supply voltage U and the load current I

$$S = U \times I$$

For customers a worth has however only
the energy delivered

$$W = \int_0^{\tau} P dt$$

The inequality

$$S > P$$


is of the major importance for electrical systems economy

By the end of XIX century
it was concluded
that

$$S^2 - P^2 = Q^2$$

where Q denotes the reactive power of the load

Steinmetz Experiment: 1892

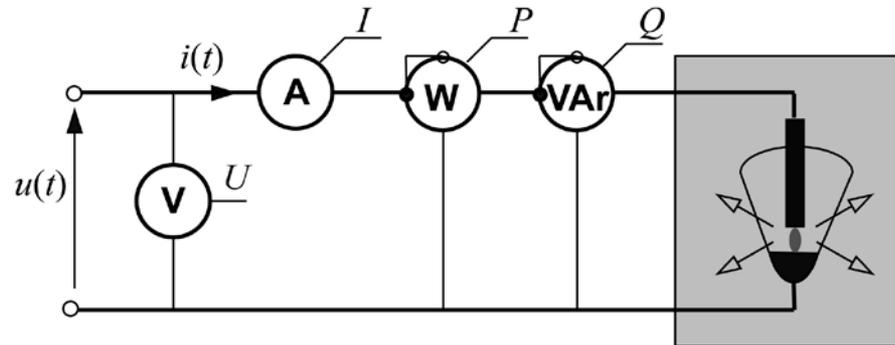

$$P^2 + Q^2 < S^2, \quad Q = 0$$

Why the apparent power S is higher than the active power P ?

How the difference between S and P can be reduced ?

**Why the apparent power S is higher
than the active power P ?**


**How the difference between S and P
can be reduced ?**

These apparently simple questions
have occurred
to be ones of the most difficult questions of electrical engineering
for the whole XX century.

Hundreds of scientists were involved
in the quest for the answer.
Hundreds of papers have been published.



Charles Proteus Steinmetz

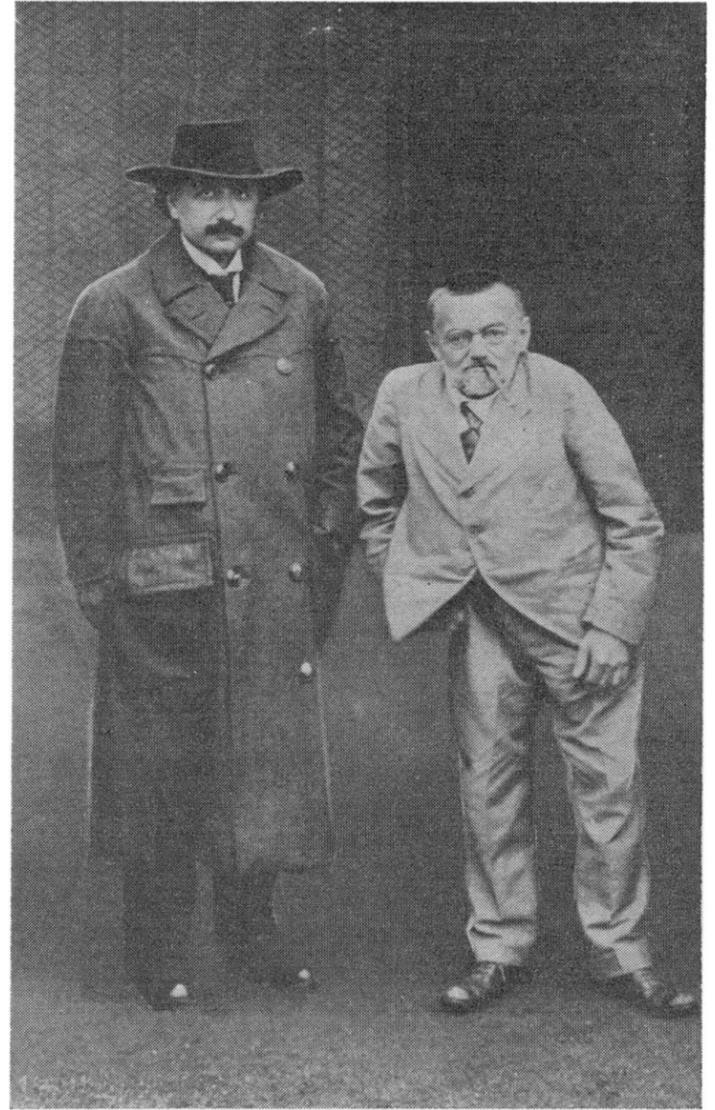


Einstein and Steinmetz.

In Einstein's company...

Present day “Steinmetz Experiment”
with line currents up to

625 kA

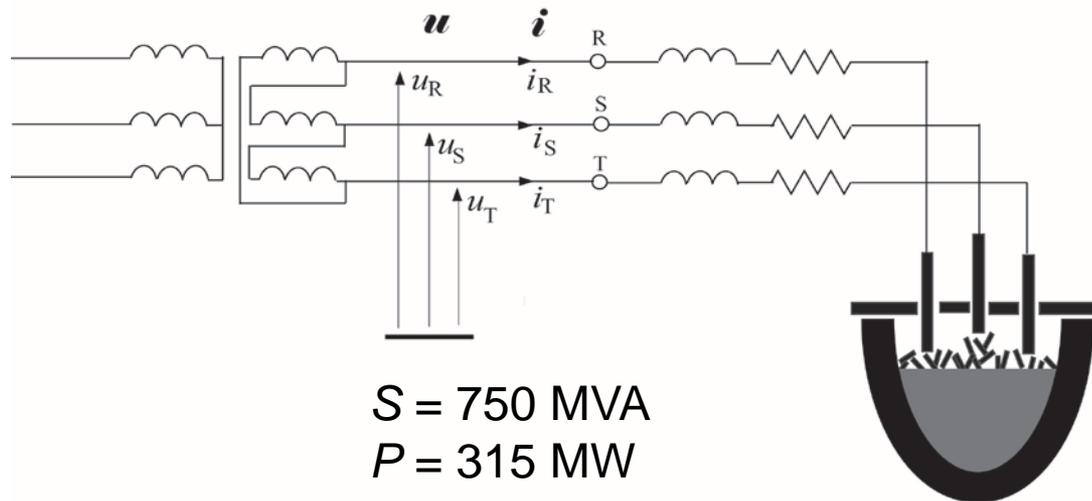

Current not only distorted, but also asymmetrical and random
Power factor: $\lambda \sim 0.42$

Annual bill for energy $\sim 500 \text{ Million } \$$

Major discussion forums:

**International Workshop on Reactive Power Definition and
Measurements in Nonsinusoidal Systems,**

Bi-annual meetings in Italy,
Chaired by A. Ferrero

**International School on Nonsinusoidal Currents and Compensation
(ISNCC)**

Bi-annual meetings in Poland
Chaired by L.S. Czarnecki

1927: Budeanu: $S^2 = P^2 + Q_B^2 + D^2$ $Q_B = \sum_{n=1}^{\infty} U_n I_n \sin \varphi_n$

**Endorsed by the IEEE Standard Dictionary of Electrical and Electronics Terms in 1992
and German Standards DIN in 1972**

1931: Fryze: $S^2 = P^2 + Q_F^2$ $Q_F = \|u\| \|i_{TF}\|$

Endorsed by German Standards DIN in 1972

1971: Shepherd: $S^2 = S_R^2 + Q_S^2$ $Q_S = \|u\| \|i_{TS}\|$


1975: Kusters: $S^2 = P^2 + Q_K^2 + Q_I^2$ $Q_K = \|u\| \|i_{TC}\|$

Endorsed by the International Electrotechnical Commission in 1980

1979: Depenbrock: $S^2 = P^2 + Q_1^2 + V^2 + N^2$

2003: Tenti: $S^2 = P^2 + Q_T^2 + D_T^2$ $Q_T = \|u\| \|i_{TT}\|$

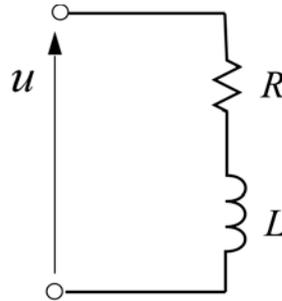Since the Steinmetz's experiment
in 1892,
by 1983, after 91 years
of Power Theory development for single-phase, LTI loads,
such as



we have had five different power equations and five different reactive powers
Compensation problem was not solved

**The problem was eventually solved
in frame of
Currents' Physical Components (CPC) – based power theory
by
L.S. Czarnecki in 1984**

This, eventually a positive result
was a conclusion
of a specific approach to the power theory development.

Its core is the concept
of


Currents' Physical Components (CPC)

**According to the CPC concept, the load current can be decomposed
into**

- 1. Mutually orthogonal components**
- 2. Associated with distinctive physical phenomena**

Currents' Physical Components (CPC)

Power Theory

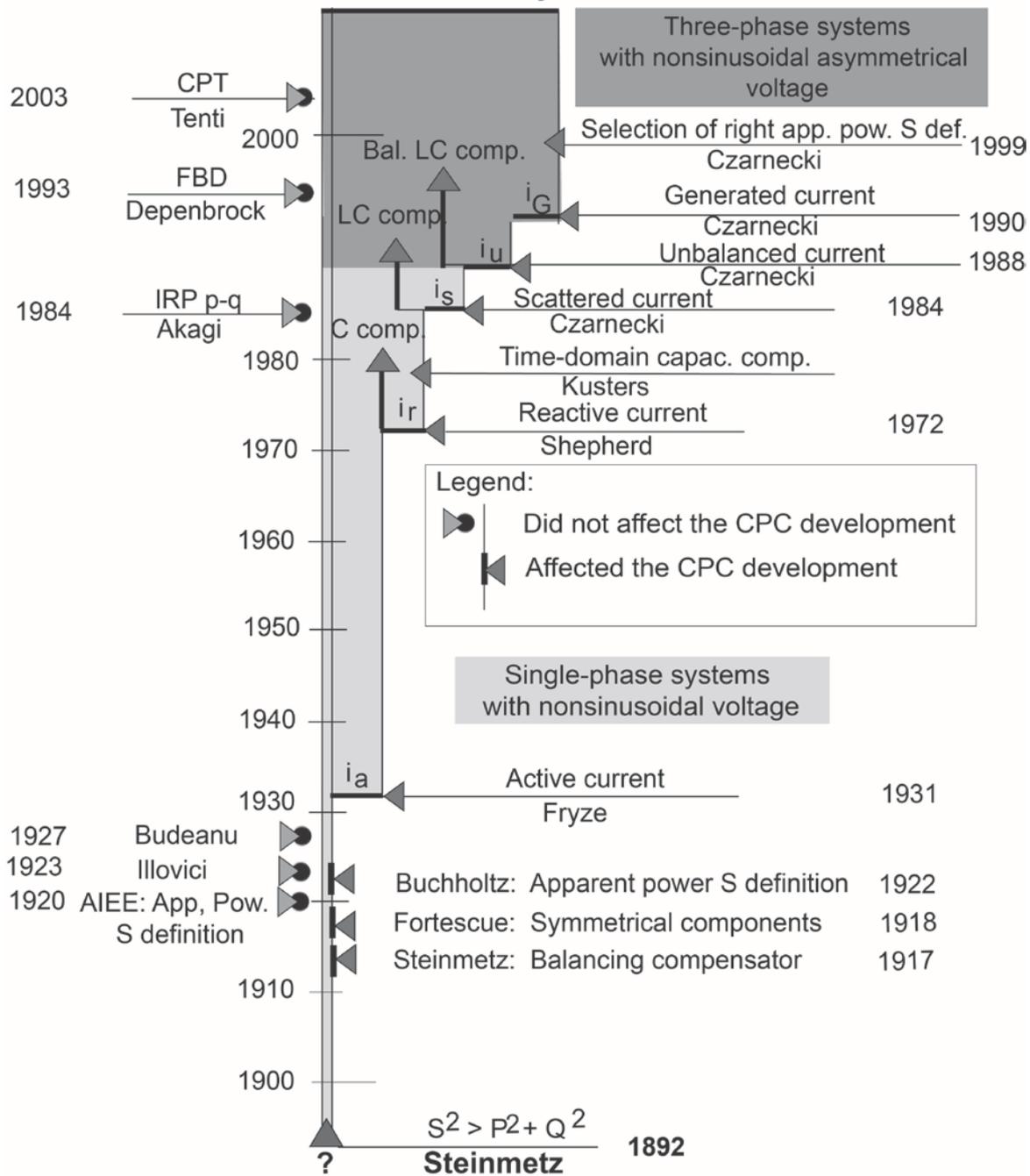

Current Physical Components (CPC) in single-phase systems with linear time-invariant loads

مؤلفه های فیزیکی جریان در سیستم های تک فاز با
بار خطی نامتغیر با زمان


L.S. Czarnecki, "**Considerations on the reactive power in nonsinusoidal situations,**" *IEEE Trans. Instr. Meas.*, Vol. IM-34, No. 3, pp. 399-404, March 1984.

L.S. Czarnecki, "**Minimization of reactive power in nonsinusoidal situation,**" *IEEE Trans. Instr. Measur.*, Vol. IM-36, No. 1, pp. 18-22, March 1987.

L.S. Czarnecki, "**Scattered and reactive current, voltage, and power in circuits with nonsinusoidal waveforms and their compensation,**" *IEEE Instr. Measur.*, Vol. 40, No. 3, pp. 563-567, June 1991.

$$u = U_0 + \sqrt{2} \operatorname{Re} \sum_{n=1}^{\infty} U_n e^{jn\omega_1 t}$$
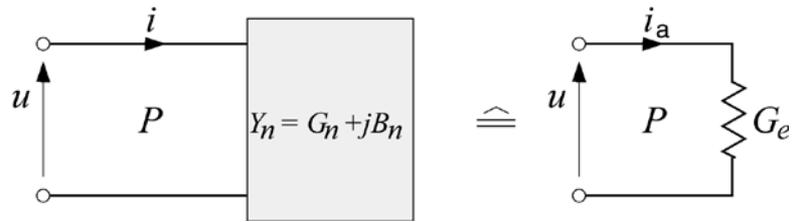
$$i = G_0 U_0 + \sqrt{2} \operatorname{Re} \sum_{n=1}^{\infty} Y_n U_n e^{jn\omega_1 t}$$



$$i = i_a + i_r + i_s$$

Fryze: (1931)	$i_a = G_e u, \quad G_e = \frac{P}{\ u\ ^2}$	Active current
Shepherd: (1971)	$i_r = \sqrt{2} \operatorname{Re} \sum_{n=1}^{\infty} jB_n U_n e^{jn\omega_1 t}$	Reactive current
Czarnecki: (1984)	$i_s = (G_0 - G_e) U_0 + \sqrt{2} \operatorname{Re} \sum_{n=1}^{\infty} (G_n - G_e) U_n e^{jn\omega_1 t}$	Scattered current

This decomposition reveals a new power phenomenon:

the existence
of the scattered current, i_s ,

that occurs when the load conductance, G_n , changes with harmonic order, n .


Current Physical Components (CPC) In single-phase systems with harmonics generating loads (HGL)

مؤلفه های فیزیکی جریان در سیستم های
تک فاز با بار مولد هارمونیک

L.S. Czarnecki, "An orthogonal decomposition of the current of nonsinusoidal voltage source applied to nonlinear loads," *Int. Journal on Circuit Theory and Appl.*, Vol. 11, pp. 235-239, 1983.

L.S. Czarnecki and T. Swietlicki, "Powers in nonsinusoidal networks, their analysis, interpretation and measurement," *IEEE Trans. Instr. Measur.*, Vol. IM-39, No. 2, pp. 340-344, April 1990.
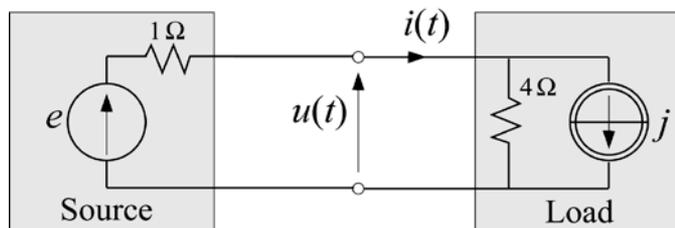
$$e = 100\sqrt{2} \sin\omega_1 t \text{ V}$$



$$j = 50\sqrt{2} \sin 3\omega_1 t \text{ A}$$

$$i = \sqrt{2}(20 \sin\omega_1 t + 40 \sin 3\omega_1 t) \text{ A} \quad \|i\| = 44.7 \text{ A}$$

$$u = \sqrt{2}(80 \sin\omega_1 t - 40 \sin 3\omega_1 t) \text{ V} \quad \|u\| = 89.4 \text{ V}$$


$$S = 4.0 \text{ kW}$$

$$P = 1600 - 1600 = 0, \quad Q = 0$$

How to write power equation for such a circuit?

This circuit reveals
that at some harmonic frequencies
the energy flows from the load back to the supply source
thus


$$P_n < 0$$

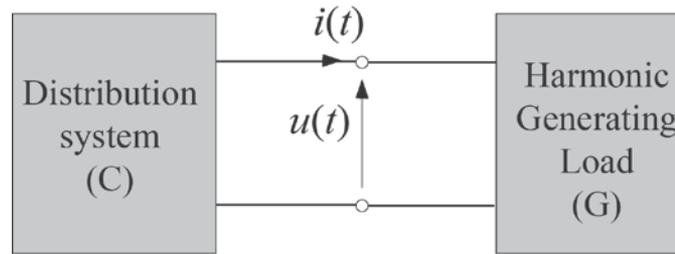


$$P_n = U_n I_n \cos\{\varphi_n\} \begin{cases} \geq 0, & n \in N_C, & \text{energy flows to the load} \\ < 0, & n \in N_G, & \text{energy flows to the supply} \end{cases}$$

Permanent flow of energy at some harmonic frequencies from the load back to the supply source can be regarded as a physical phenomenon
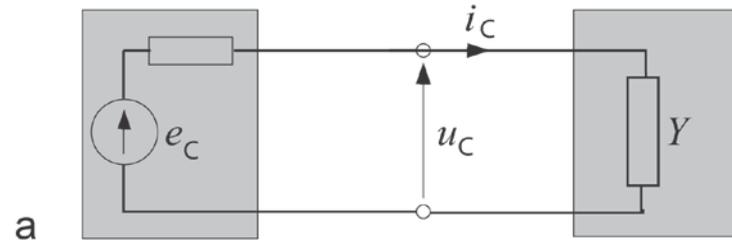
$$P_n \geq 0, \quad n \in N_C, \quad \text{energy flows to the load}$$


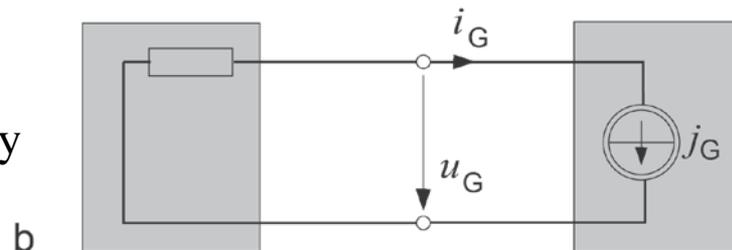
$$P_n < 0, \quad n \in N_G, \quad \text{energy flows to the supply}$$



CPC

in single-phase circuits
with Harmonics Generating Loads (HGL)

$$i(t) = i_{Ca}(t) + i_{Cr}(t) + i_{Cs}(t) + i_G(t)$$

$$i_{Ca} = G_e u_C, \quad G_{Ce} = \frac{P_C}{\|u_C\|^2} \quad \text{Active current}$$

$$i_{Cs} = \sqrt{2} \operatorname{Re} \sum_{n \in N_C} (G_n - G_{Ce}) U_n e^{jn\omega_1 t} \quad \text{Scattered current}$$


$$i_{Cr} = \sqrt{2} \operatorname{Re} \sum_{n \in N_C} jB_n U_n e^{jn\omega_1 t} \quad \text{Reactive current}$$

$$i_G = \sum_{n \in N_G} i_n \quad \text{Load generated current}$$

Current Physical Components (CPC) in three-phase systems with linear time-invariant (LTI) loads

مؤلفه های فیزیکی جریان در سیستم های سه
فاز با بار خطی نامتغیر با زمان

- L.S. Czarnecki, "Orthogonal decomposition of the current in a three-phase non-linear asymmetrical circuit with nonsinusoidal voltage," *IEEE Trans. Instr. Measur.*, Vol. IM-37, No. 1, March 1988.
- L.S. Czarnecki, "Reactive and unbalanced currents compensation in three-phase circuits under nonsinusoidal conditions," *IEEE Trans. Instr. Measur.*, Vol. IM-38, No. 3, June 1989.
- L.S. Czarnecki, "Minimization of unbalanced and reactive currents in three-phase asymmetrical circuits with nonsinusoidal voltage," *Proc. IEE*, Vol. 139, Pt. B, No. 4, July 1992.
- L.S. Czarnecki, "Power factor improvement of three-phase unbalanced loads with nonsinusoidal voltage," *European Trans. on Electrical Power Systems, ETEP*, Vol. 3, No. 1, pp. 67-74, Jan./Febr. 1993.
- L.S. Czarnecki, "Equivalent circuits of unbalanced loads supplied with symmetrical and asymmetrical voltage and their identification", *Archiv fur Elektrotechnik*, 78 1995.
- L.S. Czarnecki, "Energy flow and power phenomena in electrical circuits: illusions and reality," *Archiv fur Elektrotechnik*, (82), No. 4, pp. 10-15, 1999.

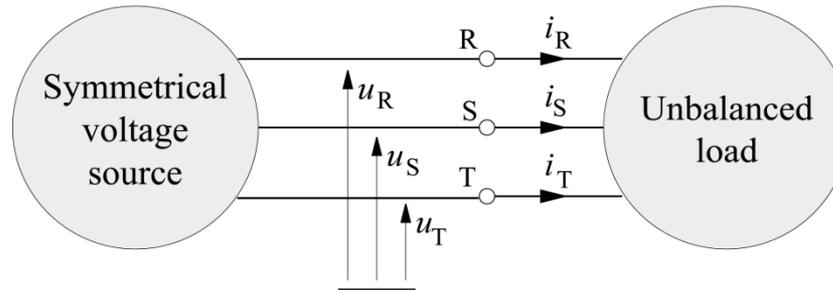


Apparent power definitions:

$$S_A = U_R I_R + U_S I_S + U_T I_T$$

$$S_G = \sqrt{P^2 + Q^2}$$

$$S_B = \sqrt{U_R^2 + U_S^2 + U_T^2} \sqrt{I_R^2 + I_S^2 + I_T^2}$$

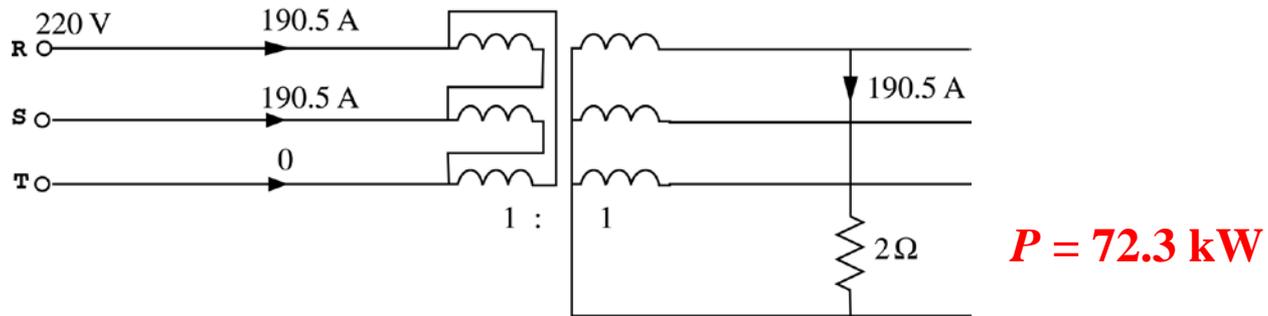Which of these three definitions is right?



$$S = S_A = U_R I_R + U_S I_S + U_T I_T = 83.8 \text{ kVA}$$

$$S = S_G = \sqrt{P^2 + Q^2} = 72.3 \text{ kVA}$$

$$S = S_B = \sqrt{U_R^2 + U_S^2 + U_T^2} \sqrt{I_R^2 + I_S^2 + I_T^2} = 220\sqrt{3} \times 190.2\sqrt{2} = 102.7 \text{ kVA}$$


$$\lambda_A = \frac{P}{S_A} = 0.86$$

$$\lambda_G = \frac{P}{S_G} = 1$$

$$\lambda_B = \frac{P}{S_B} = 0.71$$


Which of these three is the right value of the power factor?

Apparent power definition selection:

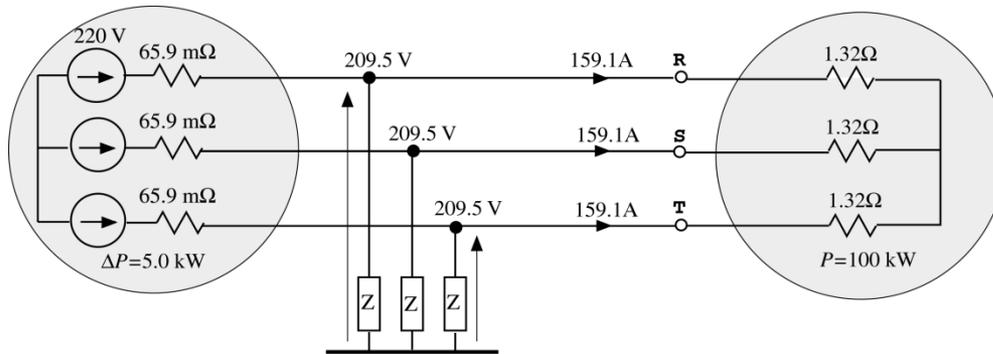

$$S_A = S_G = S_B = 100 \text{ kVA}$$
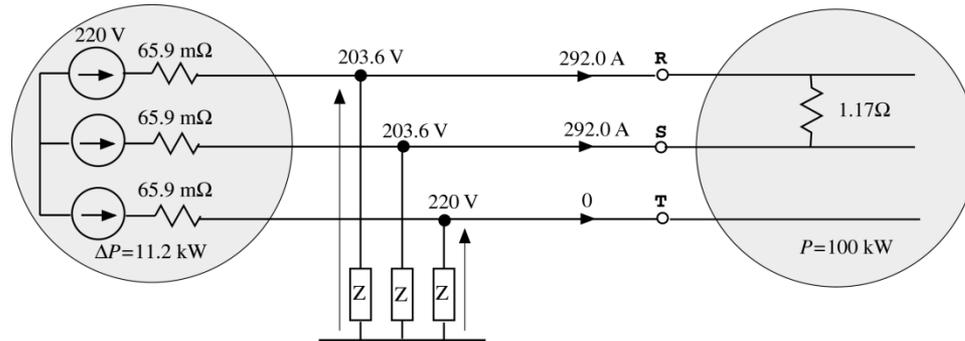
$$\lambda_A = \lambda_G = \lambda_B = 1$$



$$S_A = 119 \text{ kVA}, \quad \lambda_A = 0.84$$

$$S_G = 100 \text{ kVA}, \quad \lambda_G = 1$$


$$S_B = 149 \text{ kVA}, \quad \lambda_B = 0.67$$

Geometrical definition of the apparent power S_G results
in unity power factor in spite of increase of energy loss at delivery

The apparent power should not be calculated according to
geometrical definition

$$S_G = \sqrt{P^2 + Q^2}$$

It is wrong

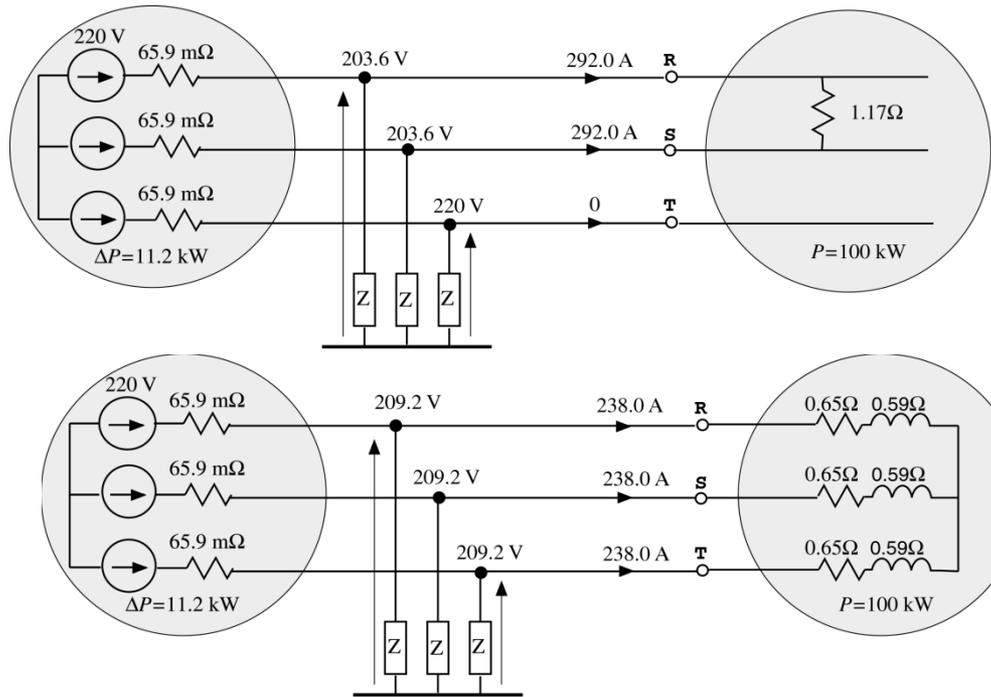

$$S_A = 119 \text{ kVA}, \quad \lambda_A = 0.84$$

$$S_G = 100 \text{ kVA}, \quad \lambda_G = 1$$


$$S_B = 149 \text{ kVA}, \quad \lambda_B = 0.67$$

$$S_A = S_G = S_B = 149 \text{ kVA}$$

$$\lambda_A = \lambda_G = \lambda_B = 0.67$$

Power loss in the supply of unbalanced load
is the same as power loss of a balanced load when the apparent power
is calculated according to formula

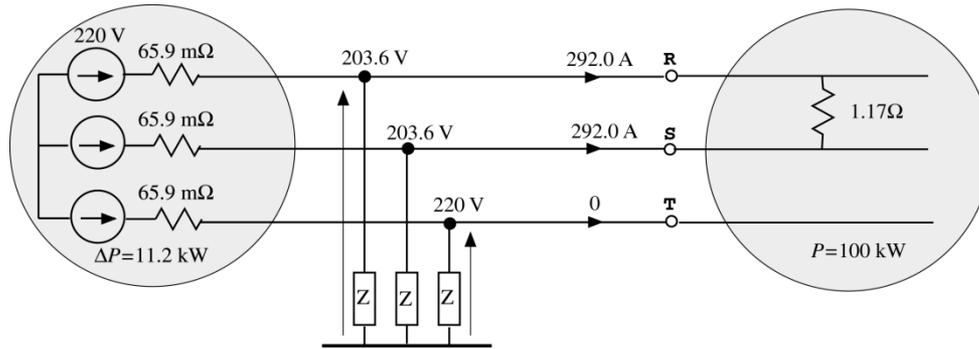
$$S = \sqrt{U_R^2 + U_S^2 + U_T^2} \sqrt{I_R^2 + I_S^2 + I_T^2}$$



$$S_A = 119 \text{ kVA}, \quad \lambda_A = 0.84$$

$$S_G = 100 \text{ kVA}, \quad \lambda_G = 1$$
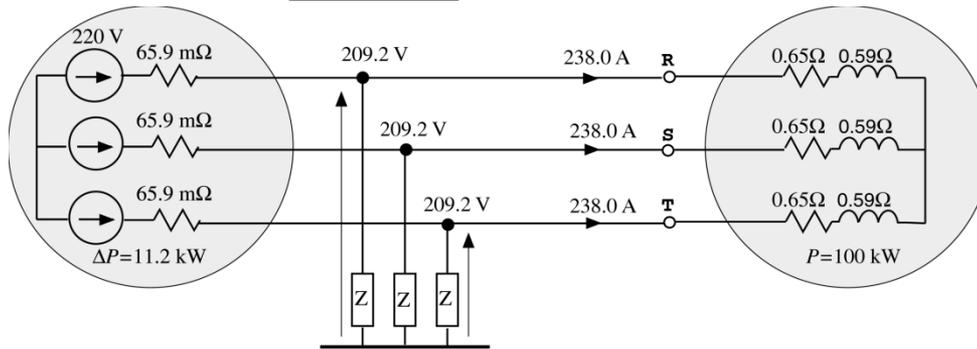
$$S_B = 149 \text{ kVA}, \quad \lambda_B = 0.67$$



$$S_A = S_G = S_B = 149 \text{ kVA}$$

$$\lambda_A = \lambda_G = \lambda_B = 0.67$$


Also arithmetical definition of the apparent power S_A results in a wrong value of the power factor.

The apparent power should not be calculated according to arithmetical definition

$$S_A = U_R I_R + U_S I_S + U_T I_T$$

It is wrong

Numerical illustration:

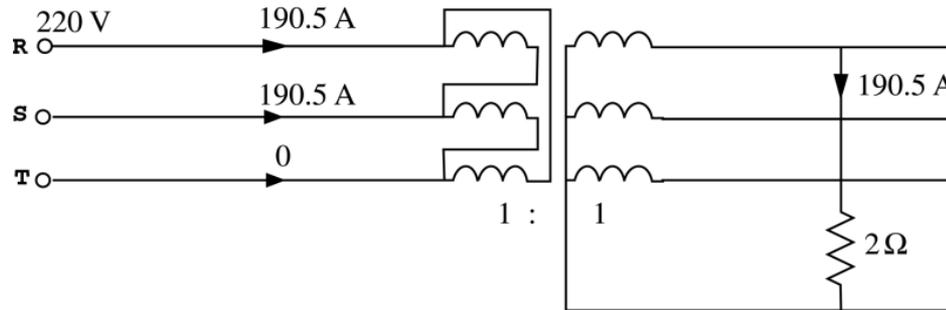

$$S = \sqrt{U_R^2 + U_S^2 + U_T^2} \sqrt{I_R^2 + I_S^2 + I_T^2} = 102.7 \text{ kVA}$$

$$P = 72.6 \text{ kW}$$

$$Q = 0$$


The relationship: $S^2 = P^2 + Q^2$ is not fulfilled by these values

This power equation is erroneous

Three phase vectors and their scalar product

Three-phase structure, combined with Fourier decomposition makes equations of three-phase nonsinusoidal systems complex and illegible

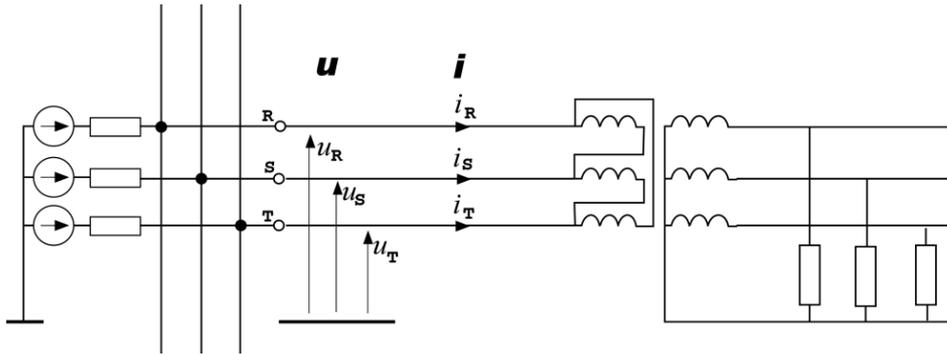More compact mathematical symbols are needed to simplify such equations



$$\mathbf{u}(t) = \begin{bmatrix} u_R(t) \\ u_S(t) \\ u_T(t) \end{bmatrix} = \mathbf{u}, \quad \mathbf{i}(t) = \begin{bmatrix} i_R(t) \\ i_S(t) \\ i_T(t) \end{bmatrix} = \mathbf{i}$$


$$P = \frac{1}{T} \int_0^T (u_R i_R + u_S i_S + u_T i_T) dt = \frac{1}{T} \int_0^T \mathbf{u}^T(t) \mathbf{i}(t) dt = (\mathbf{u}, \mathbf{i})$$

Scalar product of three-phase vectors, $\mathbf{x}(t)$ and $\mathbf{y}(t)$

$$(\mathbf{x}, \mathbf{y}) = \frac{1}{T} \int_0^T \mathbf{x}^T(t) \mathbf{y}(t) dt$$

Vectors, $\mathbf{x}(t)$ and $\mathbf{y}(t)$ are orthogonal when their scalar product $(\mathbf{x}, \mathbf{y}) = 0$

RMS value of a Three-Phase quantity

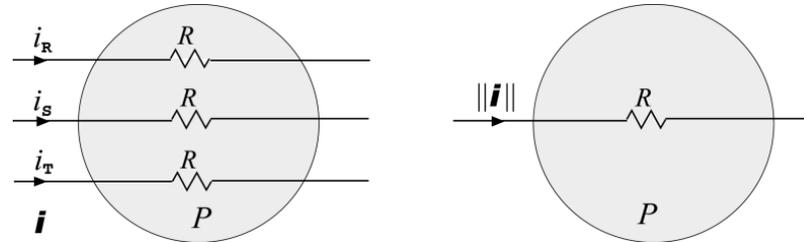

Heat released in such equipment is proportional to the active power

$$P = R \frac{1}{T} \int_0^T (i_R^2 + i_S^2 + i_T^2) dt = R \frac{1}{T} \int_0^T \mathbf{i}^T(t) \mathbf{i}(t) dt = R \sqrt{(\mathbf{i}, \mathbf{i})} = R \|\mathbf{i}\|^2$$

The quantity:

$$\|\mathbf{i}\| = \sqrt{\frac{1}{T} \int_0^T (i_R^2 + i_S^2 + i_T^2) dt} = \sqrt{\|i_R\|^2 + \|i_S\|^2 + \|i_T\|^2}$$

is the RMS value of the three phase current.


Similarly

$$\|\mathbf{u}\| = \sqrt{\frac{1}{T} \int_0^T (u_R^2 + u_S^2 + u_T^2) dt} = \sqrt{\|u_R\|^2 + \|u_S\|^2 + \|u_T\|^2}$$

is the RMS value of the three phase voltage


Apparent power

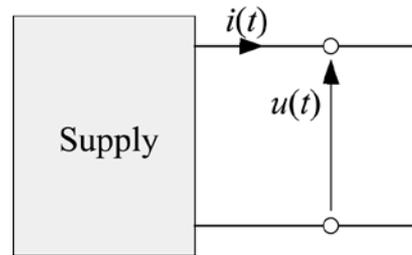Apparent power is a conventional quantity



$$S = \|u\| \|i\|$$

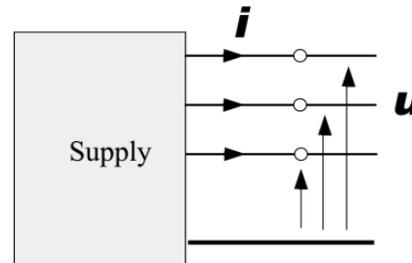Product of RMS values of the voltage and current needed for the load supply





$$S = \|u\| \|i\|$$

At sinusoidal voltages and currents

$$S = \sqrt{U_R^2 + U_S^2 + U_T^2} \sqrt{I_R^2 + I_S^2 + I_T^2}$$

CPC at sinusoidal conditions
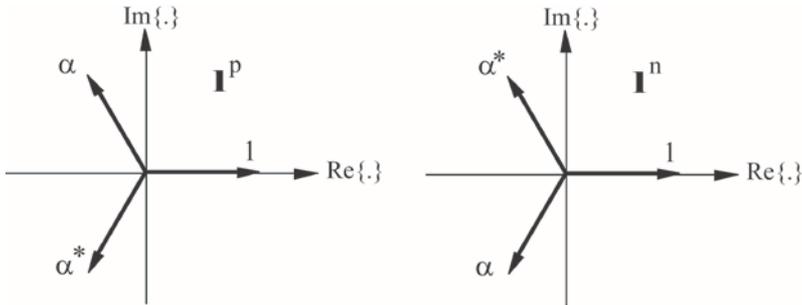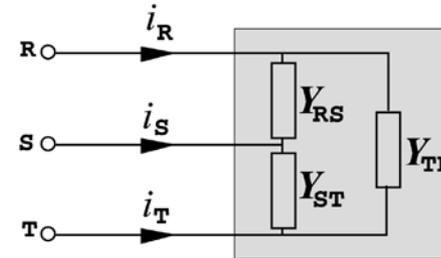
$$\mathbf{i} = \begin{bmatrix} i_R \\ i_S \\ i_T \end{bmatrix} = \sqrt{2} \operatorname{Re} \begin{bmatrix} \mathbf{I}_R \\ \mathbf{I}_S \\ \mathbf{I}_T \end{bmatrix} e^{j\omega t} = \sqrt{2} \operatorname{Re} \mathbf{I} e^{j\omega t}$$



$$I_R = (Y_{RS} + Y_{ST} + Y_{TR})U_R - (Y_{ST} + \alpha Y_{TR} + \alpha^* Y_{RS})U_S$$

$$I_S = (Y_{RS} + Y_{ST} + Y_{TR})U_S - (Y_{ST} + \alpha Y_{TR} + \alpha^* Y_{RS})U_T$$

$$I_T = (Y_{RS} + Y_{ST} + Y_{TR})U_T - (Y_{ST} + \alpha Y_{TR} + \alpha^* Y_{RS})U_R$$

$$\mathbf{i} = \sqrt{2} \operatorname{Re}\{ \mathbf{I} e^{j\omega t} \} = \sqrt{2} \operatorname{Re}\{ [1^p (G_e + jB_e)U_R + 1^n Y_u U_R] e^{j\omega t} \}$$

$$Y_e = G_e + jB_e = Y_{RS} + Y_{ST} + Y_{TR}$$

Equivalent admittance

$$Y_u = - (Y_{ST} + \alpha Y_{TR} + \alpha^* Y_{RS})$$

Unbalanced admittance

$$\mathbf{i} = \sqrt{2} \operatorname{Re}\{1 e^{j\omega t}\} = \sqrt{2} \operatorname{Re}\{[1^p(G_e + jB_e)U_R + 1^n Y_u U_R] e^{j\omega t}\}$$

CPC of three-phase LTI load at sinusoidal supply voltage

$$\mathbf{i} = \mathbf{i}_a + \mathbf{i}_r + \mathbf{i}_u$$

$$\mathbf{i}_a = \sqrt{2} \operatorname{Re}\{1^p G_e U_R e^{j\omega t}\}$$

Active current

$$\mathbf{i}_r = \sqrt{2} \operatorname{Re}\{1^p jB_e U_R e^{j\omega t}\}$$

Reactive current

$$\mathbf{i}_u = \sqrt{2} \operatorname{Re}\{1^n Y_u U_R e^{j\omega t}\}$$

Unbalanced current

The unbalanced current is associated with the phenomenon of the load current asymmetry

CPC implementation for the reactive and unbalanced currents compensation

$$\lambda = \frac{P}{S} = \frac{\|\mathbf{i}_a\|}{\sqrt{\|\mathbf{i}_a\|^2 + \|\mathbf{i}_u\|^2 + \|\mathbf{i}_r\|^2}}$$

$$\mathbf{i}_r = \sqrt{2} \operatorname{Re}\{j[B_e + (T_{ST} + T_{TR} + T_{RS})] U e^{j\omega t}\}$$

$$\mathbf{i}_u = \sqrt{2} \operatorname{Re}\{[Y_u - j(T_{ST} + \alpha T_{TR} + \alpha^* T_{RS})] U^\# e^{j\omega t}\}$$

Reactive & unbalanced currents
are compensated totally, if:

$$B_e + (T_{ST} + T_{TR} + T_{RS}) = 0$$


$$Y_u - j(T_{ST} + \alpha T_{TR} + \alpha^* T_{RS}) = 0$$

$$Y_{RSc} = jT_{RS}$$

$$Y_{STc} = jT_{ST}$$

$$Y_{TRc} = jT_{TR}$$

Solution:

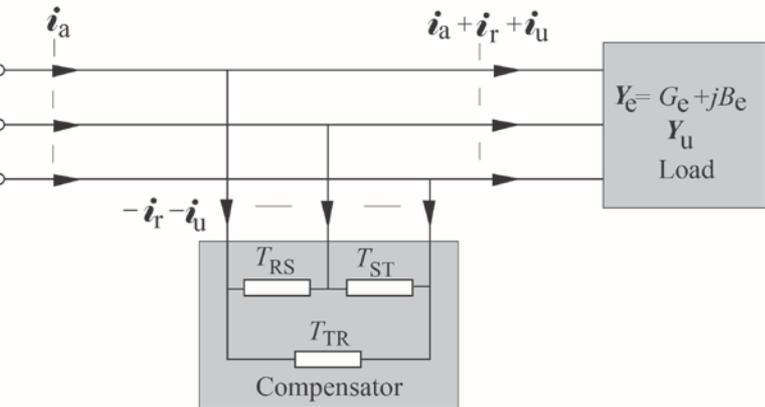


$$T_{RS} = (\sqrt{3} \operatorname{Re}\{Y_u\} - \operatorname{Im}\{Y_u\} - B_e) / 3$$

$$T_{ST} = (2 \operatorname{Im}\{Y_u\} - B_e) / 3$$

$$T_{TR} = (-\sqrt{3} \operatorname{Re}\{Y_u\} - \operatorname{Im}\{Y_u\} - B_e) / 3$$

Illustration

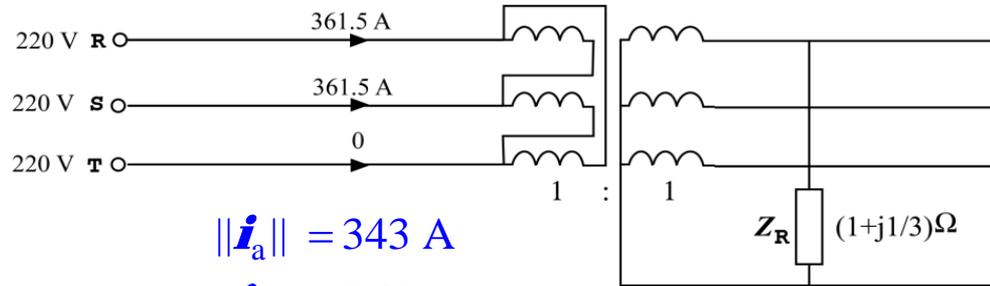

Load parameters:

$$Y_e = G_e + jB_e = Y_{RS} = 0.90 - j0.30 \text{ S}$$

$$Y_u = -\alpha * Y_{RS} = 0.95 e^{j42^\circ} = 0.71 + j0.64 \text{ S}$$

$S = 195 \text{ kVA}$

$$\|i_a\| = 343 \text{ A}$$

$$\|i_u\| = 361 \text{ A}$$

$$\|i_T\| = 114 \text{ A}$$


$$\|i\| = 511 \text{ A}$$

$$\lambda = 0.67$$

$$T_{RS} = (\sqrt{3} \text{Re} Y_u^n - \text{Im} Y_u^n - B_e) / 3 = 0.30 \text{ S}$$

$$T_{ST} = (2 \text{Im} Y_u^n - B_e) / 3 = 0.52 \text{ S}$$
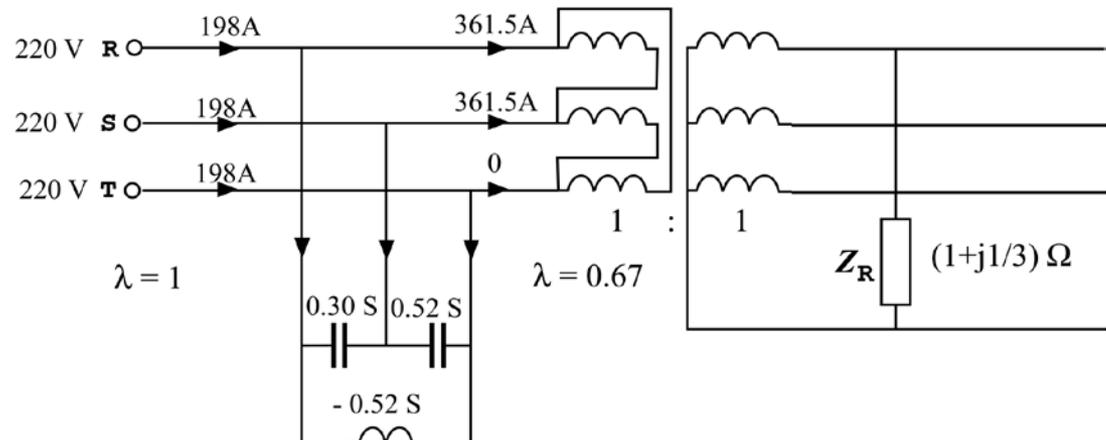
$$T_{TR} = (-\sqrt{3} \text{Re} Y_u^n - \text{Im} Y_u^n - B_e) / 3 = -0.52 \text{ S}$$



$S = 131 \text{ kVA}$

$$\|i_a\| = 343 \text{ A}$$

$$\|i_u\| = 0$$

$$\|i_T\| = 0$$

$$\|i\| = 343 \text{ A}$$

$$\lambda = 1$$

Currents' Physical Components (CPC) in three-phase systems with asymmetrical supply voltage

مؤلفه های فیزیکی جریان در سیستم های سه فاز
با منبع ولتاژ نامتقارن

L.S. Czarnecki, P. Bhattarai, “**Reactive Compensation of LTI Loads in Three-Wire Systems at Asymmetrical Voltage**”

Przegląd Elektrotechniczny, R.91, No. 12/2015, pp. 7-11.

CPC of three-phase LTI loads at asymmetrical sinusoidal supply voltage

$$\mathbf{i} = \mathbf{i}_a + \mathbf{i}_r + \mathbf{i}_u$$

$$\mathbf{i}_a = G_b \mathbf{u}$$

$$\mathbf{i}_r = B_b \mathbf{u}(t+T/4)$$

$$\mathbf{i}_u = \sqrt{2} \operatorname{Re}\{I_u e^{j\omega t}\} = \sqrt{2} \operatorname{Re}\{(Y_d U + \mathbf{I}^n Y_u^p U^p + \mathbf{I}^p Y_u^n U^n) e^{j\omega t}\}$$


$$Y_b = G_b + jB_b = \frac{P - jQ}{\|\mathbf{u}\|^2}$$

$$Y_d = \frac{2a}{1+a^2} [Y_{ST} \cos \psi + Y_{TR} \cos(\psi - \frac{2\pi}{3}) + Y_{RS} \cos(\psi + \frac{2\pi}{3})] \quad a = a e^{j\psi} = \frac{U^n}{U^p}$$


$$Y_u^p \stackrel{\text{df}}{=} -(Y_{ST} + \alpha Y_{TR} + \alpha^* Y_{RS})$$

$$Y_u^n \stackrel{\text{df}}{=} -(Y_{ST} + \alpha^* Y_{TR} + \alpha Y_{RS})$$

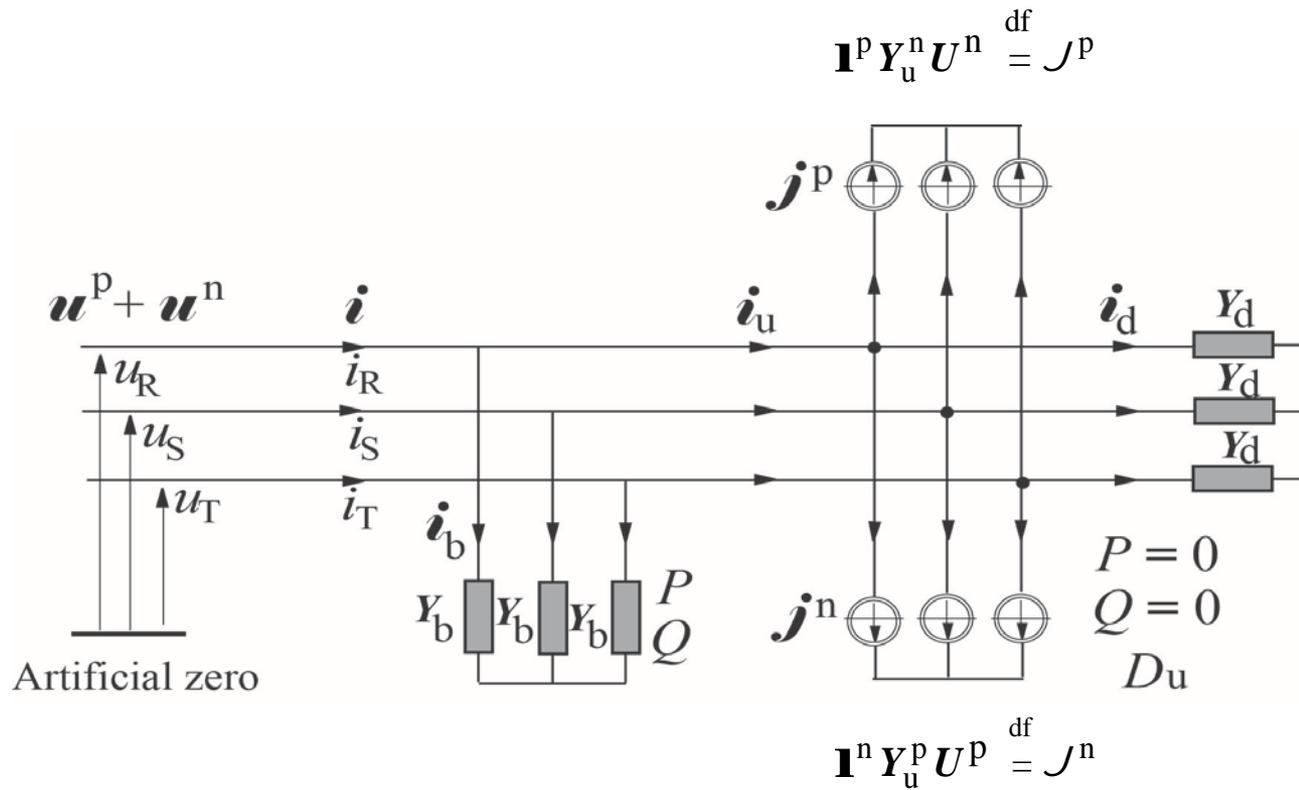Equivalent circuit of unbalanced LTI load at asymmetrical supply voltage



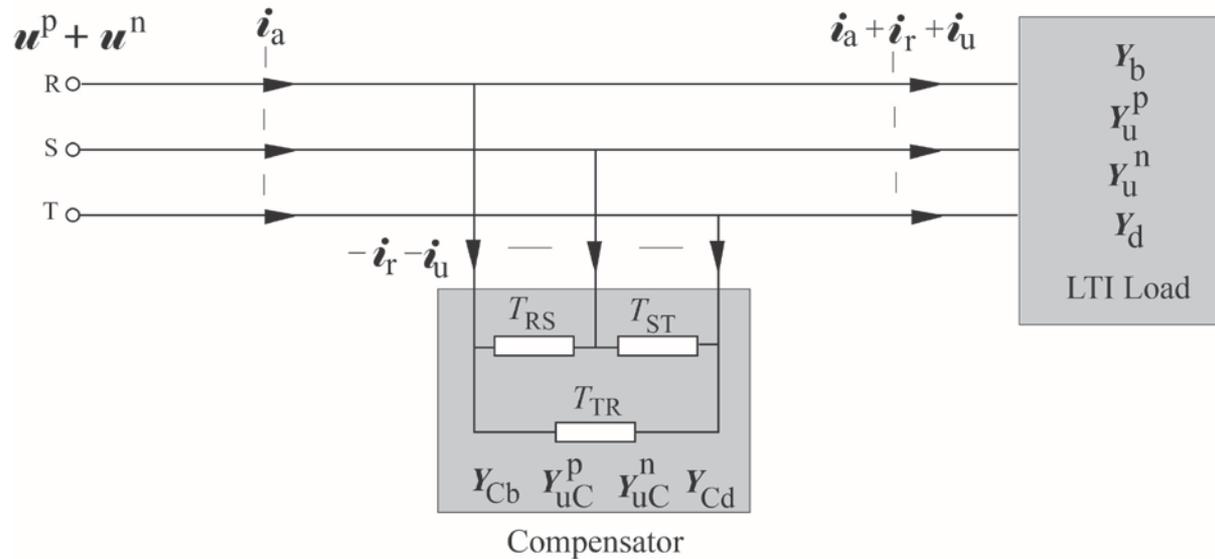CPC implementation for the reactive and the unbalanced currents compensation




$$B_{Cb} + B_b = 0 \quad (\mathbf{Y}_{Cd} + \mathbf{Y}_d)\mathbf{U} + \mathbf{1}^n(\mathbf{Y}_{uC}^p + \mathbf{Y}_u^p)\mathbf{U}^p + \mathbf{1}^p(\mathbf{Y}_{uC}^n + \mathbf{Y}_u^n)\mathbf{U}^n = 0$$


Compensator equation:

$$\begin{bmatrix} U_{RS}^2 & U_{ST}^2 & U_{TR}^2 \\ \text{Re}\mathbf{F}_1 & \text{Re}\mathbf{F}_2 & \text{Re}\mathbf{F}_3 \\ \text{Im}\mathbf{F}_1 & \text{Im}\mathbf{F}_2 & \text{Im}\mathbf{F}_3 \end{bmatrix} \begin{bmatrix} T_{RS} \\ T_{ST} \\ T_{TR} \end{bmatrix} = \begin{bmatrix} -B_b \|\mathbf{u}\|^2 \\ -\text{Re}\mathbf{F}_4 \\ -\text{Im}\mathbf{F}_4 \end{bmatrix}$$

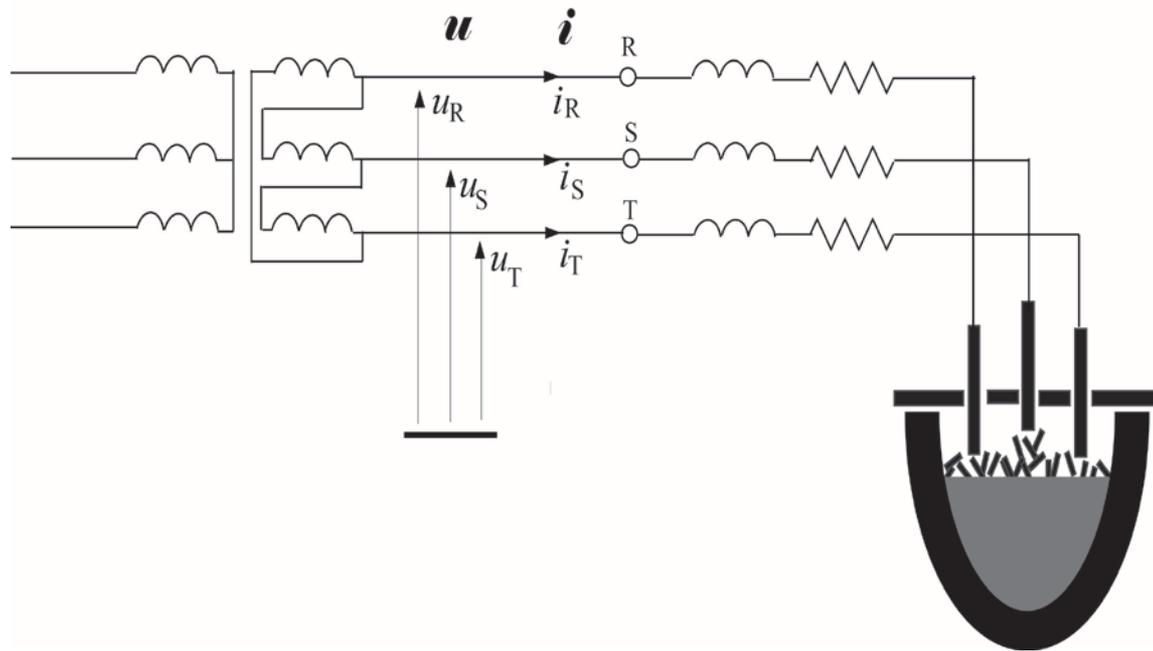
L.S. Czarnecki, P. Bhattarai, "A method of calculation of LC parameters of balancing compensators for AC arc furnaces", *IEEE Trans. on Power Delivery*, 2016



Arc furnace before compensation:

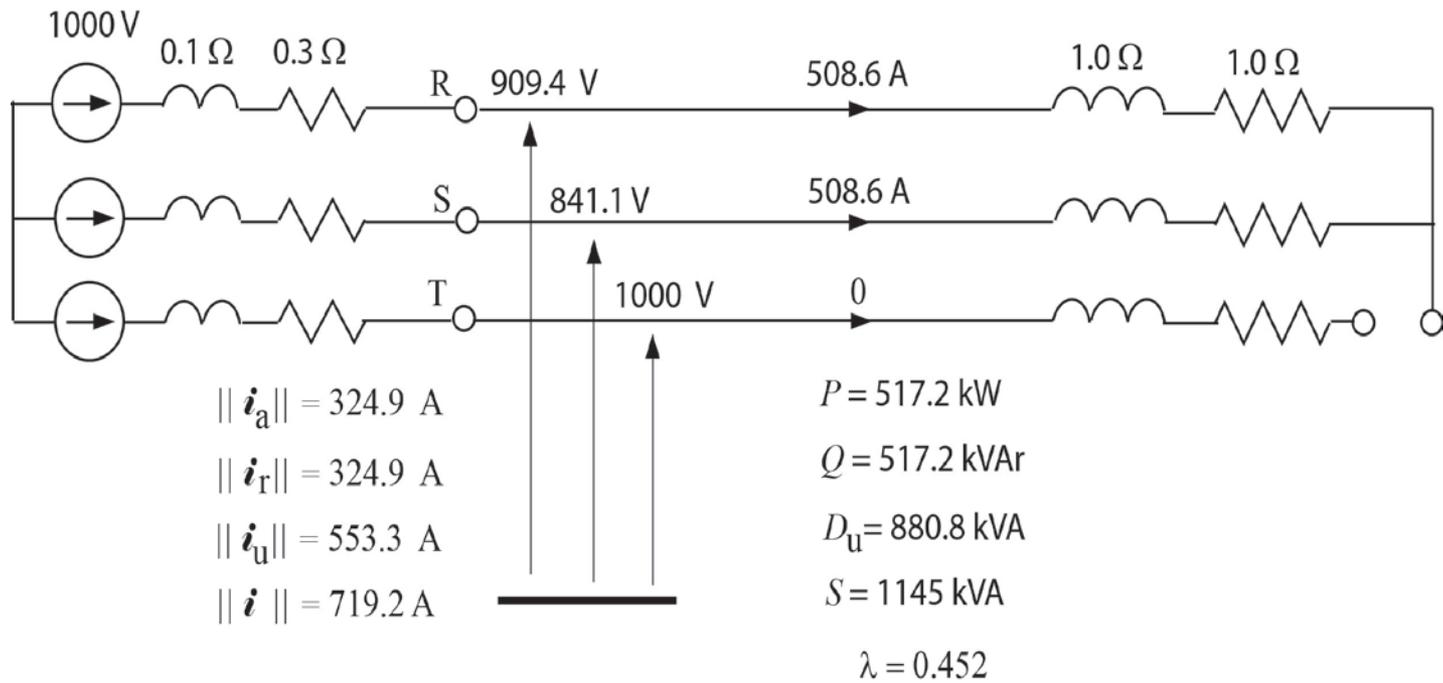

Compensation results:

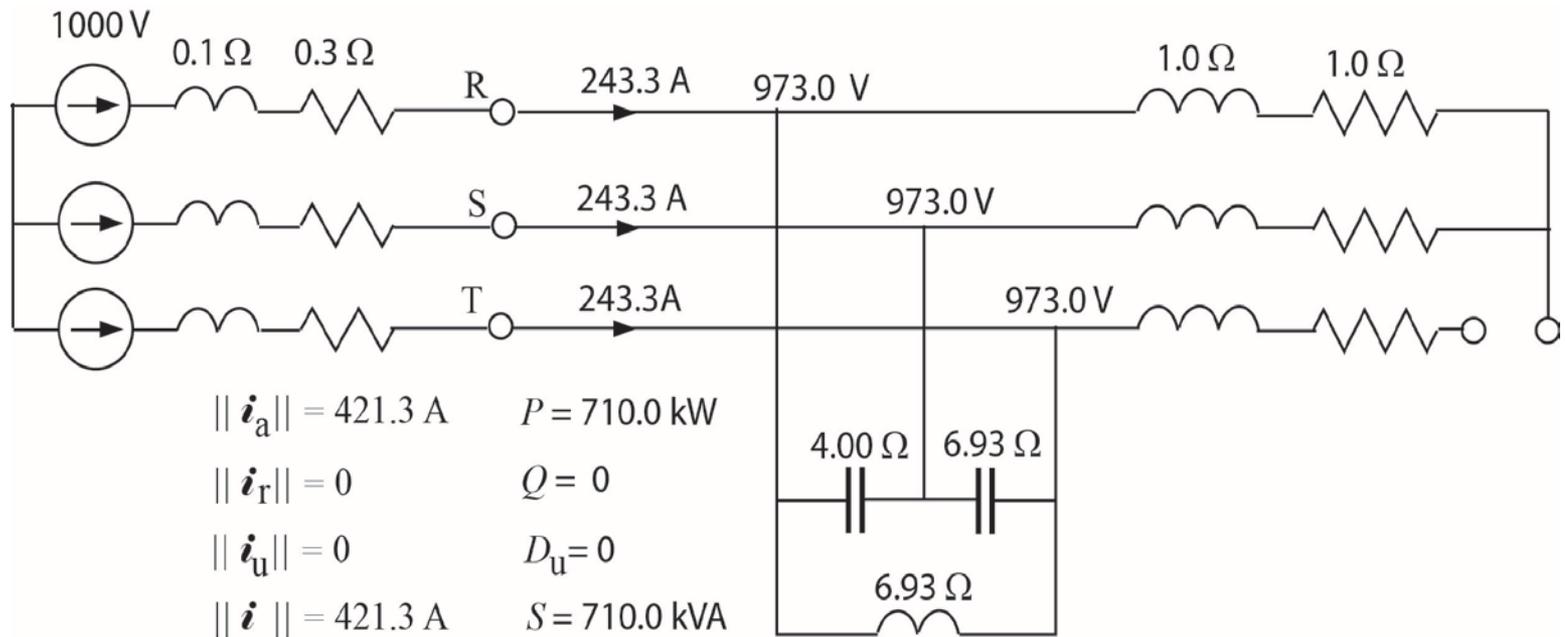

$$\lambda = 1.0$$

Current Physical Components(CPC) in linear, time-invariant (LTI) systems with symmetrical nonsinusoidal voltage

مؤلفه های فیزیکی جریان در سیستم های خطی نامتغیر با زمان
با ولتاژ متقارن غیر سینوسی

L.S. Czarnecki, "Orthogonal decomposition of the current in a three-phase non-linear asymmetrical circuit with nonsinusoidal voltage," *IEEE Trans. Instr. Measur.*, Vol. IM-37, No. 1, pp. 30-34, March 1988.

L.S. Czarnecki, "Reactive and unbalanced currents compensation in three-phase circuits under nonsinusoidal conditions," *IEEE Trans. Instr. Measur.*, Vol. IM-38, No. 3, pp. 754-459, June 1989.

$$\mathbf{u} = \sum_{n \in N} \mathbf{u}_n = \sqrt{2} \operatorname{Re} \sum_{n \in N} U_n e^{jn\omega_1 t},$$

$$\mathbf{i} = \sum_{n \in N} \mathbf{i}_n = \sqrt{2} \operatorname{Re} \sum_{n \in N} I_n e^{jn\omega_1 t}$$

CPC

of three-phase LTI loads currents at nonsinusoidal supply voltage

$$\mathbf{i} = \mathbf{i}_a + \mathbf{i}_s + \mathbf{i}_r + \mathbf{i}_u$$

Active Current:

$$\mathbf{i}_a = G_e \mathbf{u}, \quad G_e = \frac{P}{\|\mathbf{u}\|^2}$$

Scattered current:

$$\mathbf{i}_s(t) \stackrel{\text{df}}{=} \sqrt{2} \operatorname{Re} \sum_{n \in N} (G_{en} - G_e) U_n \mathbf{1}_n e^{jn\omega_1 t}$$

Reactive current:

$$\mathbf{i}_r(t) \stackrel{\text{df}}{=} \sqrt{2} \operatorname{Re} \sum_{n \in N} jB_{en} U_n \mathbf{1}_n e^{jn\omega_1 t}$$

Unbalanced current:


$$\mathbf{i}_u(t) \stackrel{\text{df}}{=} \sqrt{2} \operatorname{Re} \sum_{n \in N} Y_{un} U_n \mathbf{1}_n^* e^{jn\omega_1 t}$$

$$Y_{un} \stackrel{\text{df}}{=} -\left(Y_{STn} + e^{jn\frac{2\pi}{3}} Y_{TRn} + e^{-jn\frac{2\pi}{3}} Y_{RSn} \right) = \begin{cases} Y_{un}^p, & \text{for } n=3k+1 \\ Y_{un}^n, & \text{for } n=3k-1 \end{cases}$$

CPC implementation for the reactive and unbalanced currents compensation

$$\lambda = \frac{P}{S} = \frac{\|\mathbf{i}_a\|}{\sqrt{\|\mathbf{i}_a\|^2 + \|\mathbf{i}_s\|^2 + \|\mathbf{i}_u\|^2 + \|\mathbf{i}_r\|^2}}$$

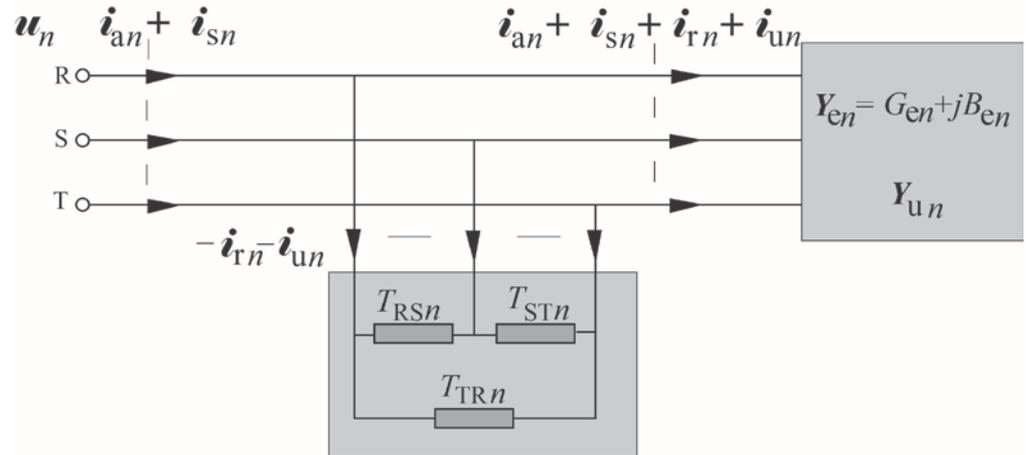Active & scattered currents are not affected by a reactive compensator




The reactive & unbalanced currents are compensated for each harmonic, if

$$B_{en} + (T_{STn} + T_{TRn} + T_{RSn}) = 0$$

$$Y_{un} - j(T_{STn} + \beta T_{TRn} + \beta^* T_{RSn}) = 0, \quad \beta = \begin{cases} \alpha & \text{for positive sequence} \\ \alpha^* & \text{for negative sequence} \end{cases}$$

From these equations the susceptances T_{RSn} , T_{STn} , and T_{TRn} , can be calculated

Example of reactive balancing:

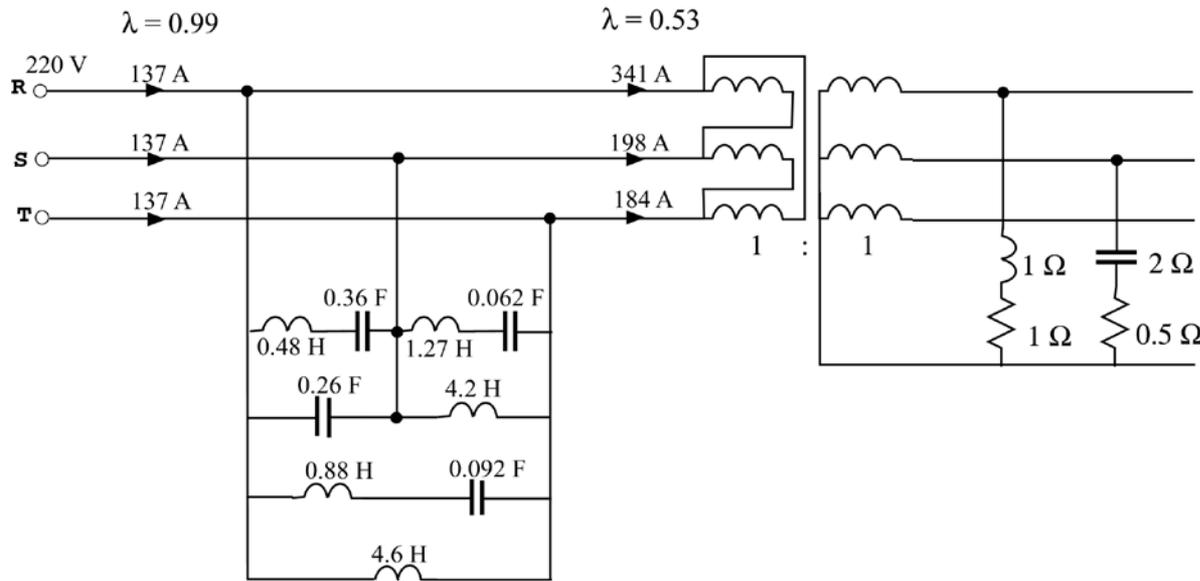

$$G_e = 0.6018 \text{ S}$$

$$Y_{e1} = 0.60 - j0.40 \text{ S}$$

$$Y_{e5} = 0.88 + j0.15 \text{ S}$$

$$Y_{u1} = 0.83 e^{-j0.18\pi} \text{ S}$$

$$Y_{u5} = 1.12 e^{-j0.86\pi} \text{ S}$$

$$\|\mathbf{i}_a\| = 237 \text{ A}$$

$$\|\mathbf{i}_s\| = 21 \text{ A}$$

$$\|\mathbf{i}_r\| = 0$$

$$\|\mathbf{i}_u\| = 0$$

$$\|\mathbf{i}\| = 238 \text{ A}$$

$$\|\mathbf{i}_a\| = 237 \text{ A}$$

$$\|\mathbf{i}_s\| = 21 \text{ A}$$

$$\|\mathbf{i}_r\| = 153 \text{ A}$$


$$\|\mathbf{i}_u\| = 327 \text{ A}$$

$$\|\mathbf{i}\| = 433 \text{ A}$$

This is an example
of a total compensation
of the reactive and unbalanced currents

CPC implementation for synthesis of reduced complexity reactive balancing compensators Illustration
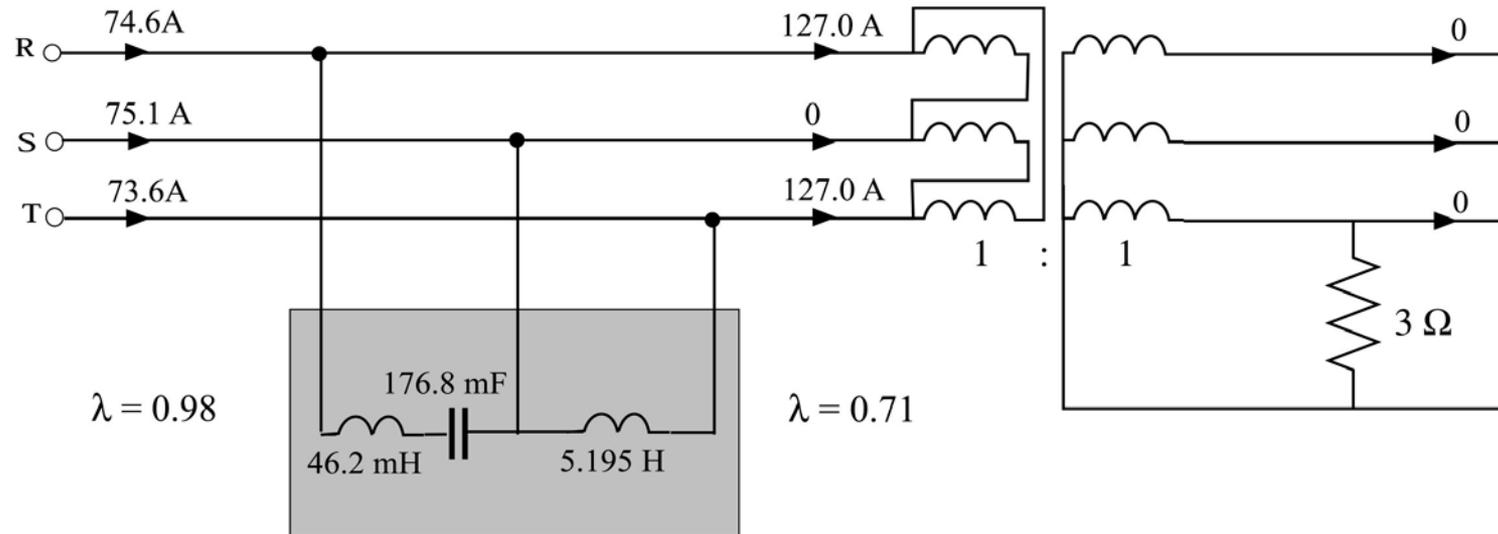
$$U_1 = 220 \text{ V} \quad U_5 = 5\%U_1 \quad U_7 = 3\%U_1$$



CPC of three-phase LTI loads with asymmetrical and nonsinusoidal voltages

(28)

$$\mathbf{i} = \mathbf{i}_a + \mathbf{i}_s + \mathbf{i}_r + \mathbf{i}_u$$

Active Current:
$$\mathbf{i}_a \stackrel{\text{df}}{=} G_b \mathbf{u} = \sqrt{2} \operatorname{Re} \sum_{n \in N} G_b U_n e^{jn\omega_1 t}$$

Scattered current:
$$\mathbf{i}_s \stackrel{\text{df}}{=} \sqrt{2} \operatorname{Re} \sum_{n \in N} (G_{bn} - G_b) U_n e^{jn\omega_1 t}$$

Reactive current:
$$\mathbf{i}_r \stackrel{\text{df}}{=} \sum_{n \in N} \mathbf{i}_{rn} = \sqrt{2} \operatorname{Re} \sum_{n \in N} jB_{bn} U_n e^{jn\omega_1 t}$$

Unbalanced current:
$$\mathbf{i}_u \stackrel{\text{df}}{=} \sqrt{2} \operatorname{Re} \sum_{n \in N} (Y_{dn} U_n + {}^1n Y_{un}^p U_n^p + {}^1p Y_{un}^n U_n^n) e^{jn\omega_1 t}$$

(With harmonic order n neglected for simplicity:)

$$\mathbf{Y}_d = 2 \frac{\mathbf{Y}_{ST} \operatorname{Re}\{W\} + \mathbf{Y}_{TR} \operatorname{Re}\{\alpha^* W\} + \mathbf{Y}_{RS} \operatorname{Re}\{\alpha W\}}{U^p{}^2 + U^n{}^2}, \quad W = U^p{}^* U^n$$

$$\mathbf{Y}_u^p \stackrel{\text{df}}{=} -(\mathbf{Y}_{ST} + \alpha \mathbf{Y}_{TR} + \alpha^* \mathbf{Y}_{RS})$$


$$\mathbf{Y}_u^n \stackrel{\text{df}}{=} -(\mathbf{Y}_{ST} + \alpha^* \mathbf{Y}_{TR} + \alpha \mathbf{Y}_{ST})$$

CPC implementation for reactive balancing compensator synthesis at asymmetrical voltage

$$E_{R1} = E_{S1} = 100 \text{ V}, \quad E_{T1} = 50 \text{ V},$$

distorted with harmonics of $n = 1, 3, 7$ of the rms value

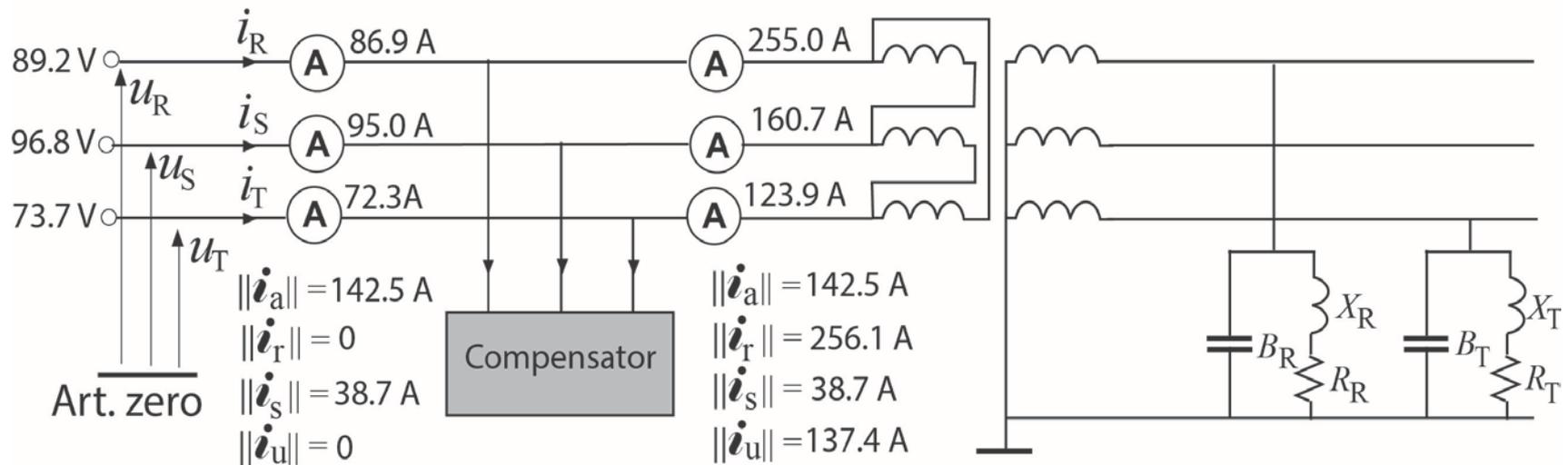
$$E_{R3} = E_{R5} = E_{R7} = 20 \text{ V}$$



CPC implementation
for synthesis of a compensator
that minimizes the reactive and unbalanced currents
at asymmetrical & nonsinusoidal voltage and non-zero source impedance

$$E_{S1} = 0.97E_{R1}, \quad E_T = 0.97E_{R1}, \quad E_3 = E_5 = E_7 = 4\% \text{ of } E_1 = 100 \text{ V}$$


$$S_{sc}/P = 20$$

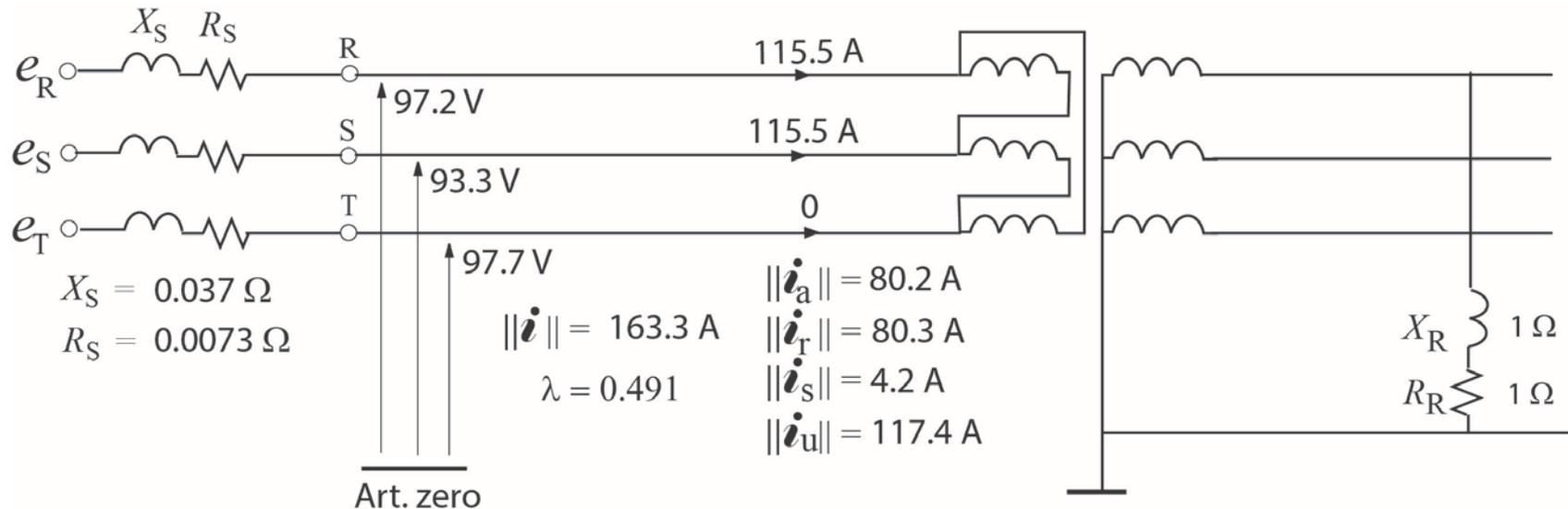

CPC implementation
for synthesis of a compensator
that minimizes the reactive and unbalanced currents
at asymmetrical & nonsinusoidal voltage and non-zero source impedance


$$E_{S1} = 0.97E_{R1}, \quad E_T = 0.97E_{R1}, \quad E_3 = E_5 = E_7 = 4\% \text{ of } E_1 = 100 \text{ V}$$

$$S_{sc}/P = 20$$

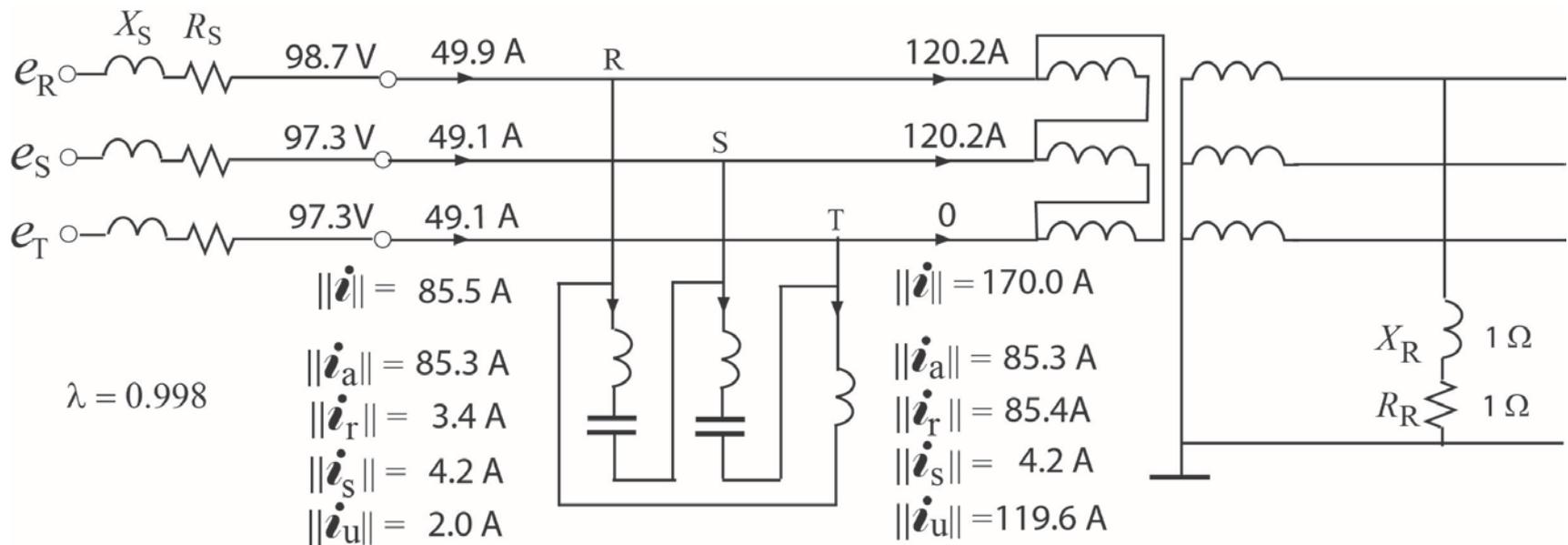

Current Physical Components (CPC) of three-phase four-wire supplied LTI loads with sinusoidal symmetrical voltage

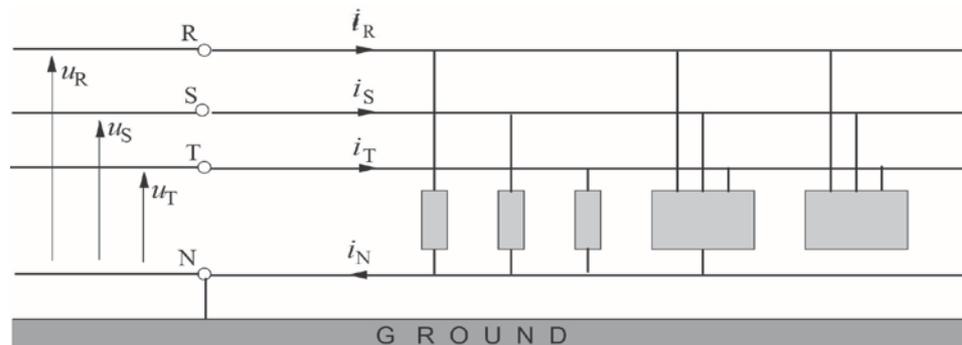مولفه های فیزیکی جریان در سیستم های سه فاز چهارسیمه با
بار خطی نامتغیر با زمان




L.S. Czarnecki, P.M. Haley, “**Power properties of four-wire systems at nonsinusoidal supply voltage**,” IEEE Trans. on Power Delivery, Vol. 31, No. 2, 2016, pp. 513-521.

L.S. Czarnecki, P.M. Haley, “**Unbalanced power in four-wire systems and its reactive compensation**”, IEEE Trans. on Power Delivery, Vol. 30, No. 1, Feb. 2015, pp. 53-63.

L.S. Czarnecki, P.H. Haley, “**Currents’ Physical Components (CPC) in Four-Wire Systems with Nonsinusoidal Symmetrical Voltage**,” *Przełąd Elektrotechniczny* R.91, No. 6/2015, pp. 48-53.

Currents' Physical Components

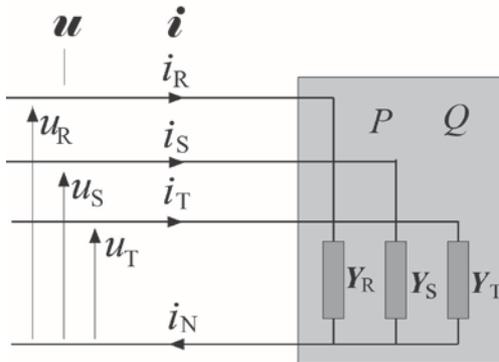

$$Y_e = G_e + jB_e = \frac{P - jQ}{\|\mathbf{u}\|^2} = \frac{1}{3}(Y_R + Y_S + Y_T)$$

$$Y_u^n \stackrel{\text{df}}{=} \frac{1}{3}(Y_R + \alpha Y_S + \alpha^* Y_T)$$

$$Y_u^z \stackrel{\text{df}}{=} \frac{1}{3}(Y_R + \alpha^* Y_S + \alpha Y_T)$$

$$\mathbf{i} = \mathbf{i}_a + \mathbf{i}_r + \mathbf{i}_u^n + \mathbf{i}_u^z$$

$$\mathbf{i}_a(t) = G_e \mathbf{u}(t)$$

Active Current:

$$\mathbf{i}_r(t) = B_e \frac{d}{d(\omega t)} \mathbf{u}(t).$$

Reactive current:


$$\mathbf{i}_u^n \stackrel{\text{df}}{=} \sqrt{2} \text{Re}\{1^n Y_u^n U_R e^{j\omega t}\}$$

Unbalanced current of negative sequence:


$$\mathbf{i}_u^z \stackrel{\text{df}}{=} \sqrt{2} \text{Re}\{1^z Y_u^z U_R e^{j\omega t}\}.$$

Unbalanced current of zero sequence

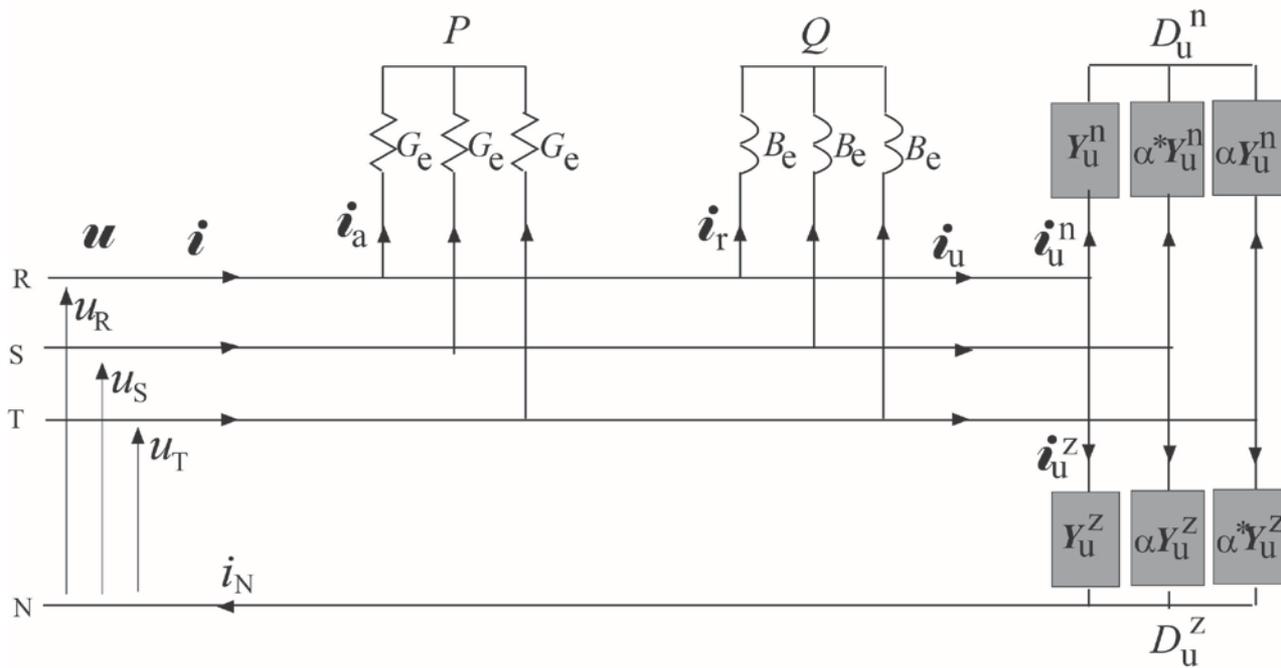CPC-based equivalent circuit of four-wire supplied loads



Numerical illustration

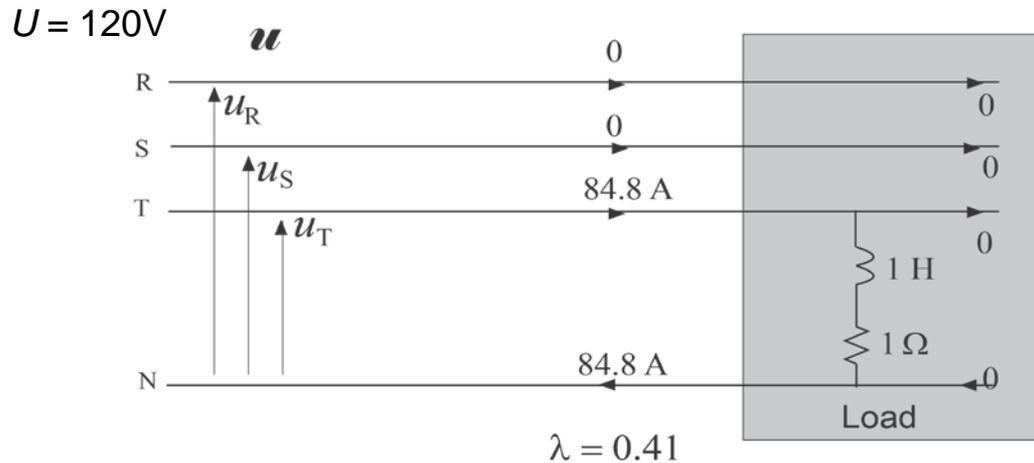

$$Y_e = G_e + jB_e = \frac{1}{3}(Y_R + Y_S + Y_T) = 0.167 - j0.167 \text{ S}$$

$$Y_u^n = \frac{1}{3}(Y_R + \alpha Y_S + \alpha^* Y_T) = 0.236 e^{-j165^\circ} \text{ S}$$

$$Y_u^z = \frac{1}{3}(Y_R + \alpha^* Y_S + \alpha Y_T) = 0.236 e^{j75^\circ} \text{ S}$$

$$\|\mathbf{u}\| = \sqrt{3}U_R = \sqrt{3} \times 120 = 207.8 \text{ V}$$


$$\|\mathbf{i}_a\| = G_e \|\mathbf{u}\| = 0.167 \times 207.8 = 34.7 \text{ A}$$

$$\|\mathbf{i}_r\| = |B_e| \|\mathbf{u}\| = 0.167 \times 207.8 = 34.7 \text{ A}$$

$$\|\mathbf{i}_u^n\| = Y_u^n \|\mathbf{u}\| = 0.236 \times 207.8 = 49.0 \text{ A}$$

$$\|\mathbf{i}_u^z\| = Y_u^z \|\mathbf{u}\| = 0.236 \times 207.8 = 49.0 \text{ A}$$

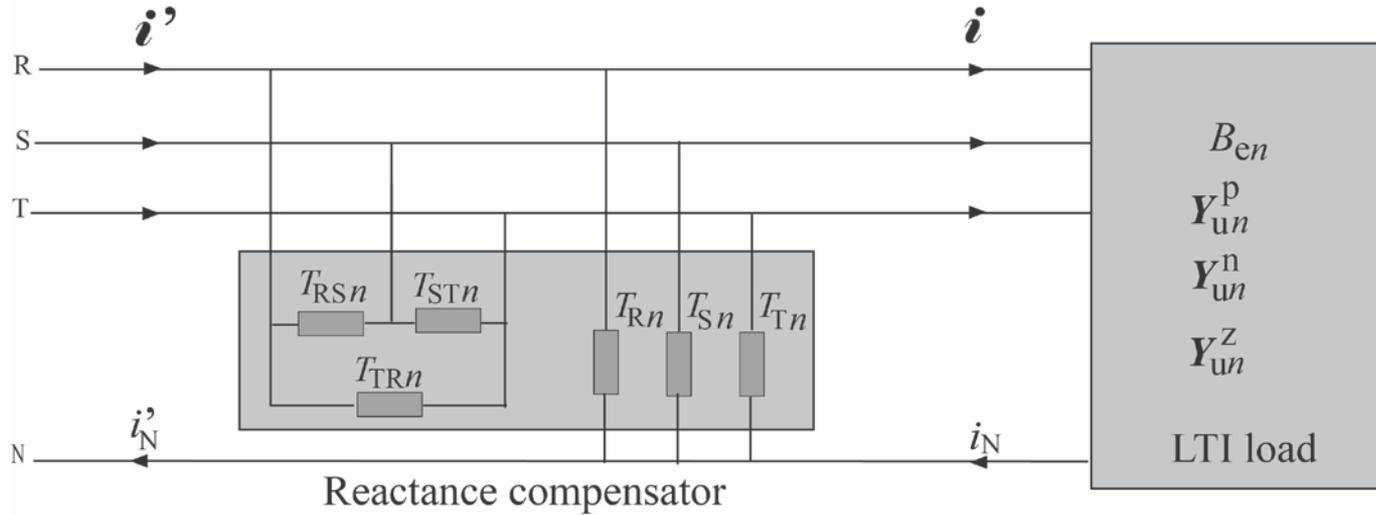CPC implementation for balancing compensator synthesis



$$\mathbf{i}'_u \equiv 0 \quad \text{if } j(T_{ST} + \alpha T_{TR} + \alpha^* T_{RS}) + \mathbf{Y}_u'^n = 0$$

$$T_{RS} = (\sqrt{3} \operatorname{Re} \mathbf{Y}_u'^n - \operatorname{Im} \mathbf{Y}_u'^n) / 3$$

$$T_{ST} = (2 \operatorname{Im} \mathbf{Y}_u'^n) / 3$$

$$T_{TR} = (-\sqrt{3} \operatorname{Re} \mathbf{Y}_u'^n - \operatorname{Im} \mathbf{Y}_u'^n) / 3$$

$$\mathbf{i}'_r \equiv 0 \quad \text{if } \frac{1}{3}(T_R + T_S + T_T) + B_e = 0$$

$$\mathbf{i}'_u \equiv 0 \quad \text{if } \frac{1}{3} j(T_R + \alpha^* T_S + \alpha T_T) + \mathbf{Y}_u^z = 0$$

$$T_R = -2 \operatorname{Im} \mathbf{Y}_n^z - B_e$$

$$T_S = -\sqrt{3} \operatorname{Re} \mathbf{Y}_n^z + \operatorname{Im} \mathbf{Y}_n^z - B_e$$

$$T_T = \sqrt{3} \operatorname{Re} \mathbf{Y}_n^z + \operatorname{Im} \mathbf{Y}_n^z - B_e.$$

Compensator of zero sequence unbalanced current

$$T_R = -2\text{Im}Y_n^Z - B_e = -0.289 \text{ S}$$

$$T_S = -\sqrt{3}\text{Re}Y_n^Z + \text{Im}Y_n^Z - B_e = 0.289 \text{ S}$$

$$T_T = \sqrt{3}\text{Re}Y_n^Z + \text{Im}Y_n^Z - B_e = 0.50 \text{ S}$$

$$Y_u'^n = Y_u^{z*} + Y_u^n = (0.061 + j0.228)^* - 0.228 - j0.061 = -0.167 - j0.289 \text{ S}$$


Compensator of negative sequence unbalanced current

$$T_{RS} = (\sqrt{3}\text{Re}Y_u'^n - \text{Im}Y_u'^n)/3 = 0$$

$$T_{ST} = (2\text{Im}Y_u'^n)/3 = -0.192 \text{ S}$$

$$T_{TR} = (-\sqrt{3}\text{Re}Y_u'^n - \text{Im}Y_u'^n)/3 = 0.192 \text{ S}$$

+ $\|i_g\|^2$

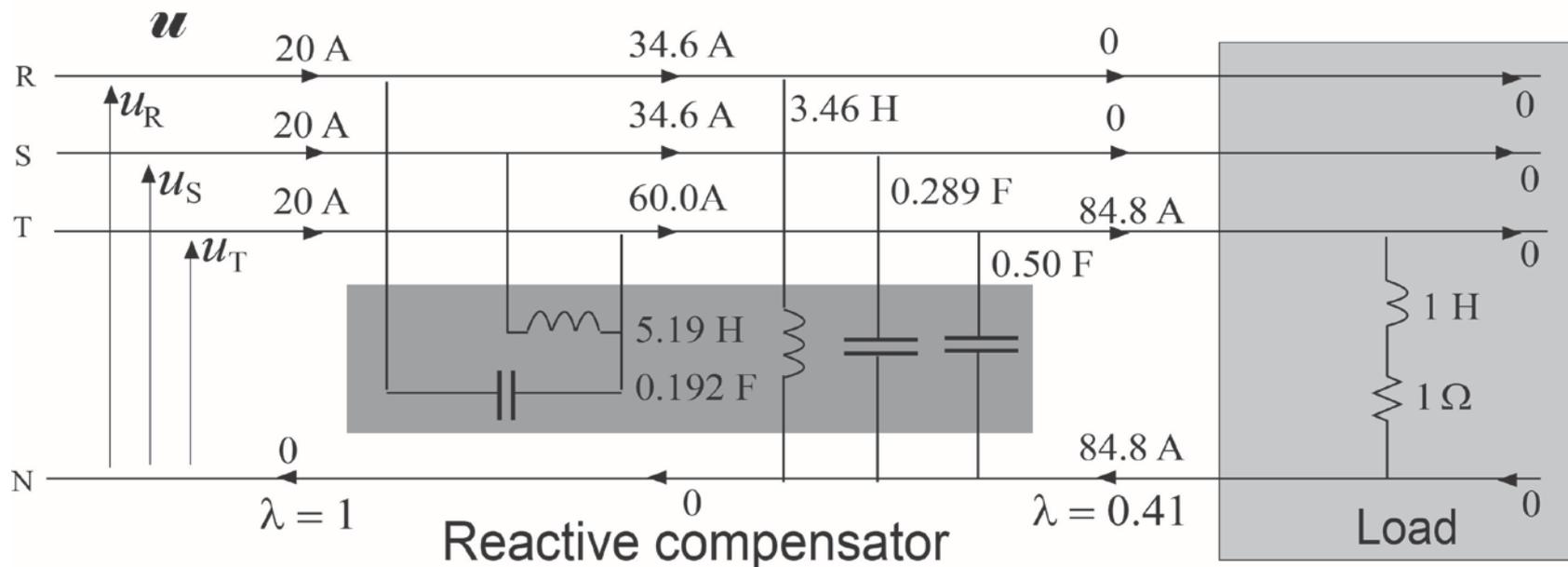

CPC
of three-phase Harmonics Generating Loads (HGL)
supplied by a four-wire line
with nonsinusoidal and asymmetrical voltages:

$$\mathbf{i}(t) = \mathbf{i}_{Ca}(t) + \mathbf{i}_{Cr}(t) + \mathbf{i}_{Cs}(t) + \mathbf{i}_{Cu}^n(t) + \mathbf{i}_{Cu}^p(t) + \mathbf{i}_{Cu}^z(t) + \mathbf{i}_G(t)$$

These currents are associated
with distinctive physical phenomena in the load

All of them
are mutually orthogonal
so that their three-phase RMS value
satisfy the relationship

$$\|\mathbf{i}\|^2 = \|\mathbf{i}_{Ca}\|^2 + \|\mathbf{i}_{Cr}\|^2 + \|\mathbf{i}_{Cs}\|^2 + \|\mathbf{i}_{Cu}^n\|^2 + \|\mathbf{i}_{Cu}^p\|^2 + \|\mathbf{i}_{Cu}^z\|^2 + \|\mathbf{i}_G\|^2$$

Various approaches to the Power Theory development

Two main approaches to the power theory development:

- Frequency-domain

- Time-domain

have competed for the whole period of its development

Prof. Budeanu (1927),
suggesting the reactive power definition:



$$Q_B \stackrel{\text{df}}{=} \sum_{n=1}^{\infty} U_n I_n \sin \varphi_n$$

**attempted to develop the power theory
in the frequency-domain**

Prof. Fryze (1931)
suggested that power theory
should be developed

without use of the concept of harmonics

Fryze's circuit:

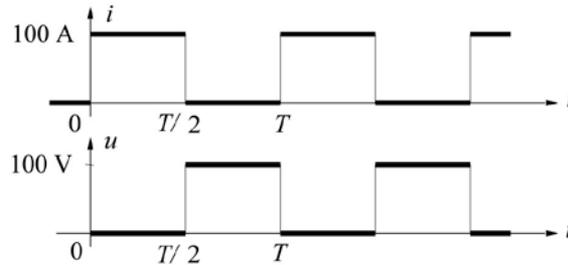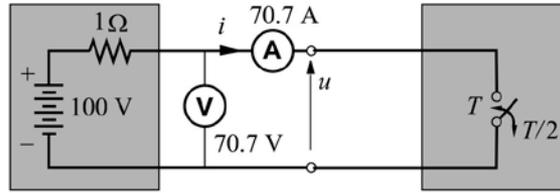

Frequency-domain:

$$u(t) = U_0 + \sqrt{2} \sum_{n=1}^{\infty} U_n \cos(n\omega_1 t + \alpha_n) = \sum_{n=0}^{\infty} u_n$$

$$i(t) = I_0 + \sqrt{2} \sum_{n=1}^{\infty} I_n \cos(n\omega_1 t + \beta_n) = \sum_{n=0}^{\infty} i_n$$

$$p(t) = \frac{dW}{dt} = u(t) i(t) = \sum_{r=0}^{\infty} u_r \sum_{s=0}^{\infty} i_s = \sum_{n=0}^{\infty} S_n \cos(n\omega_1 t + \psi_n) = ?$$

Time-domain:

$$p(t) = \frac{dW}{dt} = u(t) i(t) = 0$$

was the main Fryze's argument against the frequency-domain

The Currents' Physical Components (CPC) – Power Theory,
which is currently

the most advanced concept of the power theory of electrical systems

was formulated

in the frequency-domain

There is also a debate on,
should the power theory be developed
based on

- **instantaneous approach**
- or
- **averaged approach**

?

The Instantaneous Reactive Power p-q Theory,
developed
by Akagi, Nabae, Kanazawa


is the main example of the instantaneous approach

Circuit #1

$$u_R = \sqrt{2} U \cos \omega t, \quad U = 220 \text{ V}$$

$$i_R = \sqrt{2} I \cos(\omega t + 30^\circ), \quad I = 95.3 \text{ A}$$

$$Q = 0$$

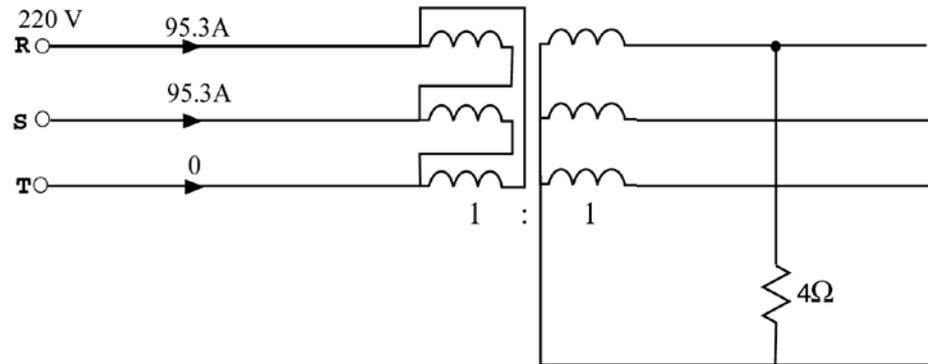

$$\begin{bmatrix} u_\alpha \\ u_\beta \end{bmatrix} = C \begin{bmatrix} u_R \\ u_S \end{bmatrix} = \begin{bmatrix} \sqrt{3} U \cos \omega t \\ \sqrt{3} U \sin \omega t \end{bmatrix}$$

$$\begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = C \begin{bmatrix} i_R \\ -i_R \end{bmatrix} = \begin{bmatrix} \sqrt{3} I \cos(\omega t + 30^\circ) \\ -I \cos(\omega t + 30^\circ) \end{bmatrix}$$

Instantaneous powers,

Active: $p = u_\alpha i_\alpha + u_\beta i_\beta = \sqrt{3} U I [1 + \cos 2(\omega t + 30^\circ)]$

Reactive: $q = u_\alpha i_\beta - u_\beta i_\alpha = -\sqrt{3} U I \sin 2(\omega t + 30^\circ)$


For $2(\omega t + 30^\circ) = 90^\circ$, $p = -q$

Circuit #2

$$u_R = \sqrt{2} U \cos \omega t, \quad U = 220 \text{ V}$$

$$i_R = \sqrt{2} I \cos(\omega t - 60^\circ), \quad I = 95.3 \text{ A}$$

$$P = 0$$

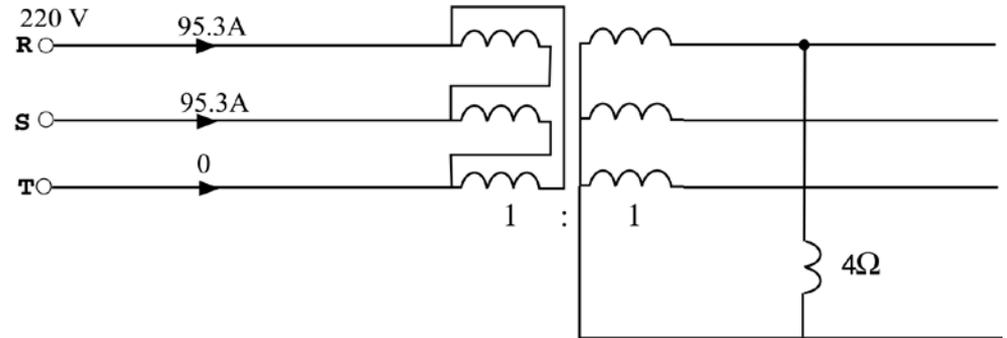

$$\begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = C \begin{bmatrix} i_R \\ -i_R \end{bmatrix} = \begin{bmatrix} \sqrt{3} I \cos(\omega t - 60^\circ) \\ -I \cos(\omega t - 60^\circ) \end{bmatrix}$$

Instantaneous powers,

Active: $p = u_\alpha i_\alpha + u_\beta i_\beta = \sqrt{3} U I [\cos(2\omega t - 30^\circ)]$

Reactive: $q = u_\alpha i_\beta - u_\beta i_\alpha = -\sqrt{3} U I [1 + \sin(2\omega t - 30^\circ)]$

For $2\omega t - 30^\circ = 0$, $p = -q$


Circuit #3

$$u_R = \sqrt{2} U \cos \omega t, \quad U = 220 \text{ V}$$

$$i_R = \sqrt{2} I \cos(\omega t - 60^\circ), \quad I = 190.5 \text{ A}$$

$$i_S = \sqrt{2} I \cos(\omega t + 60^\circ)$$

$$P = 0, \quad Q = 0$$

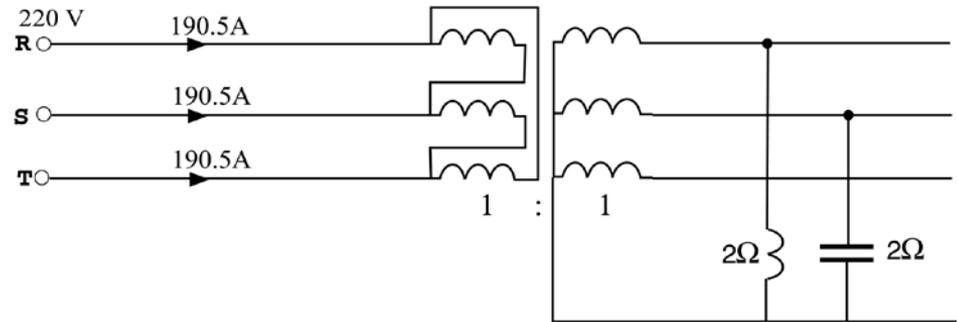

$$\begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = C \begin{bmatrix} i_R \\ i_S \end{bmatrix} = \begin{bmatrix} \sqrt{3} I \cos(\omega t - 60^\circ) \\ -\sqrt{3} I \sin(\omega t - 60^\circ) \end{bmatrix}$$

Instantaneous powers,

$$\text{Active:} \quad p = u_\alpha i_\alpha + u_\beta i_\beta = 3UI \cos(2\omega t - 60^\circ)$$

$$\text{Reactive:} \quad q = u_\alpha i_\beta - u_\beta i_\alpha = -3UI \sin(2\omega t - 60^\circ)$$

$$\text{For } 2\omega t - 60^\circ = 45^\circ, \quad p = -q$$

There are instants of time with identical pairs
of instantaneous powers p and q

$$p = -q$$


for entirely different loads

**Power properties of the load cannot be identified
instantaneously**

L.S. Czarnecki, "On some misinterpretations of the Instantaneous Reactive Power p-q Theory," IEEE Trans. on Power Electronics, Vol. 19, No.3, pp. 828-836, 2004.


L.S. Czarnecki, "Comparison of the Instantaneous Reactive Power, p-q, Theory with Theory of Current's Physical Components," *Archiv fur Elektrotechnik*, Vol. 85, No. 1, Feb. 2004, pp. 21-28.

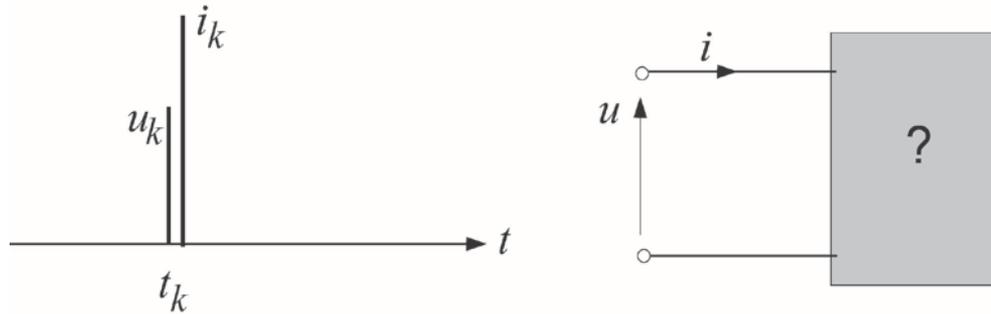Let us have a pair of instantaneous values
of voltages and currents



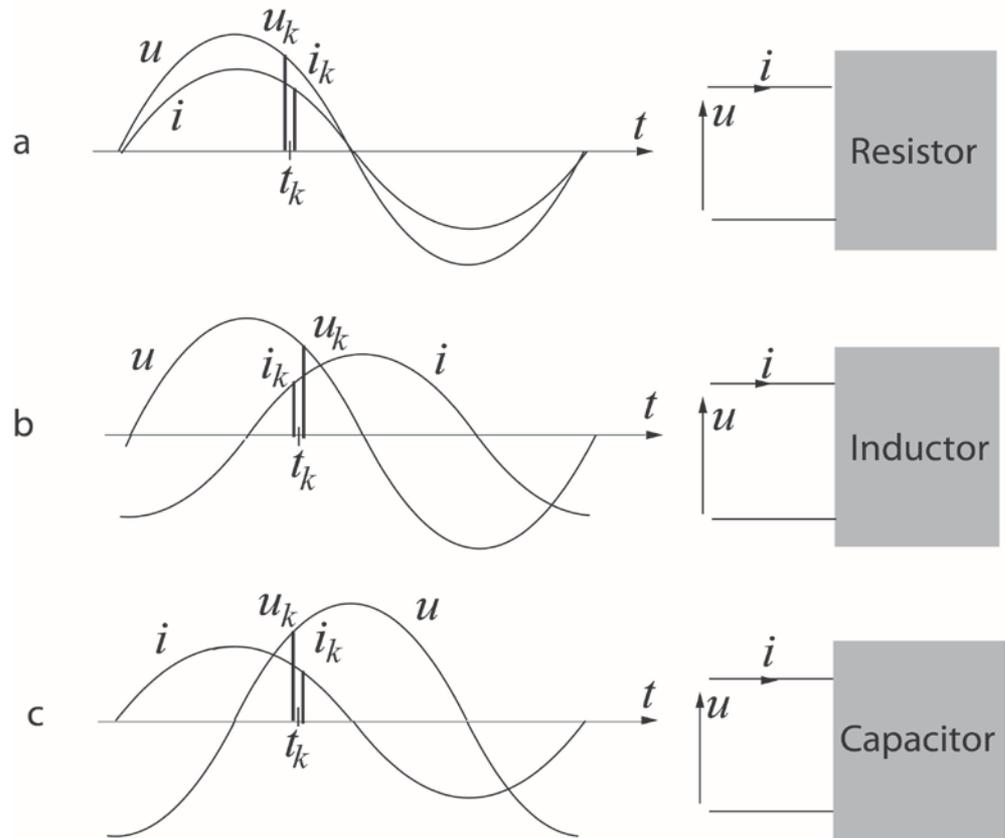Question:

What it is in the box: resistor, inductor or capacitor?



A pair of instantaneous values of voltages and current does not enable us to determine the load properties

To determine the load properties, these pairs have to be observed for the whole period T


Instantaneous approach does not provide
right fundamentals
for the power theory development

Therefore,
the CPC – based Power Theory was formulated on
an averaging approach

Compensation

The CPC-based Power Theory
is the only theory
that provides fundamentals for reactive compensator synthesis
(as demonstrated previously)

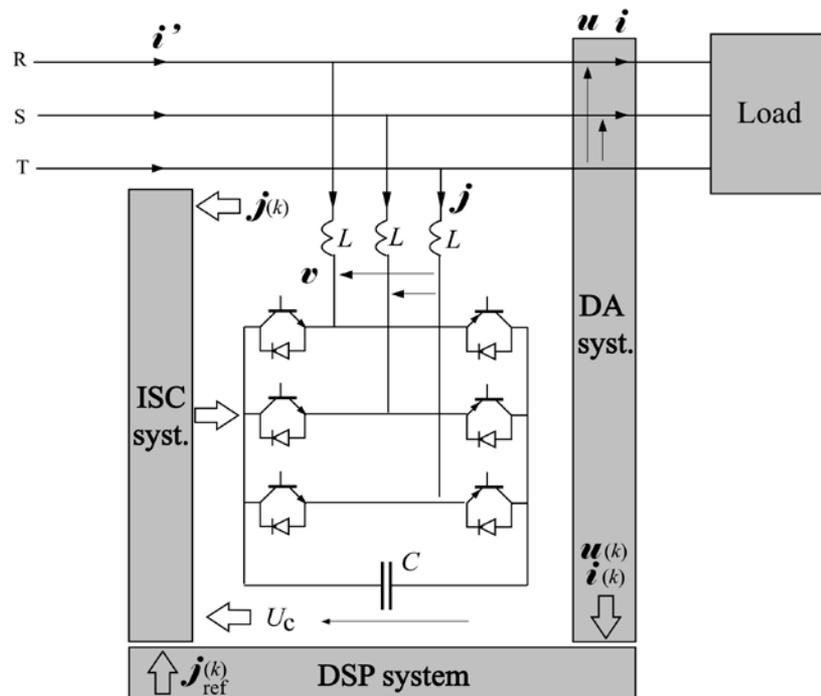as well as
it enables control
of switching compensators, known as “active power filters”



The CPC-based Power Theory
is the only theory
that provides fundamentals for reactive compensator synthesis

because
the current physical components are expressed in the CPC
in terms of the load parameters

it enables control of switching compensators

because
each component of the load current, other than the active one

$$i_{Cr}, i_{Cs}, i_{Cu}^n, i_{Cu}^p, i_{Cu}^z, i_G$$

can be regarded as a reference signal for a compensator control

Harmful Currents' Physical Components:



$$i_{Cr}, i_{Cs}, i_{Cu}^n, i_{Cu}^p, i_{Cu}^z, i_G$$

can be
measured/calculated
from measurement of voltages and currents
at the load terminals.



They differ as to properties
and a compensator needed for their reduction

They can be compensated together or
individually
by hybrid compensators


Example of a low quality load

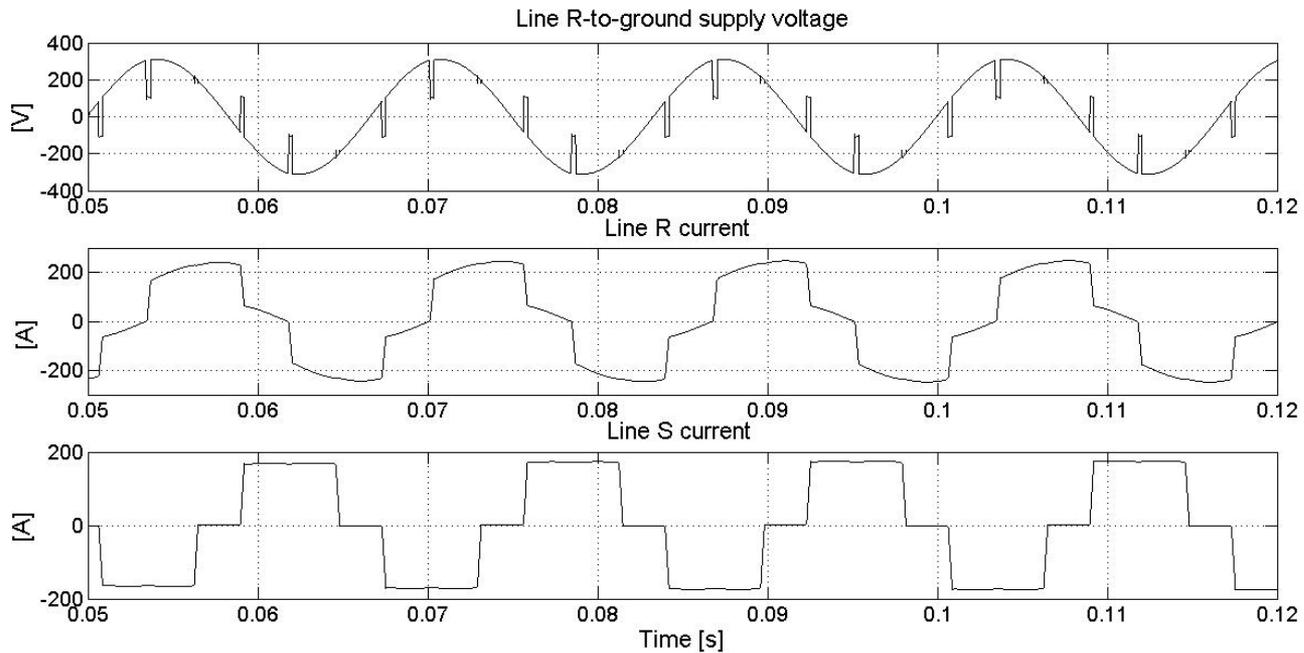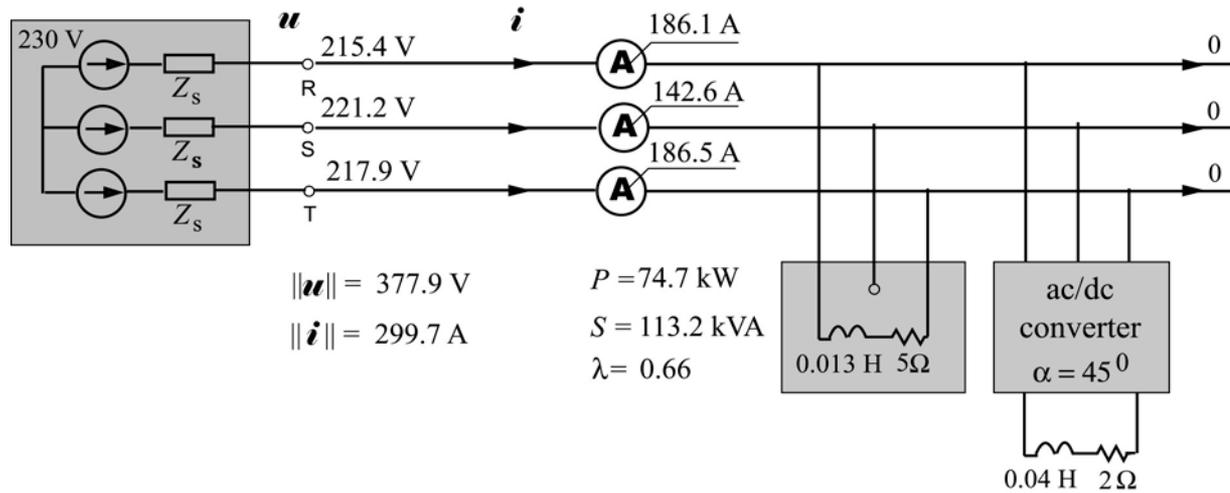

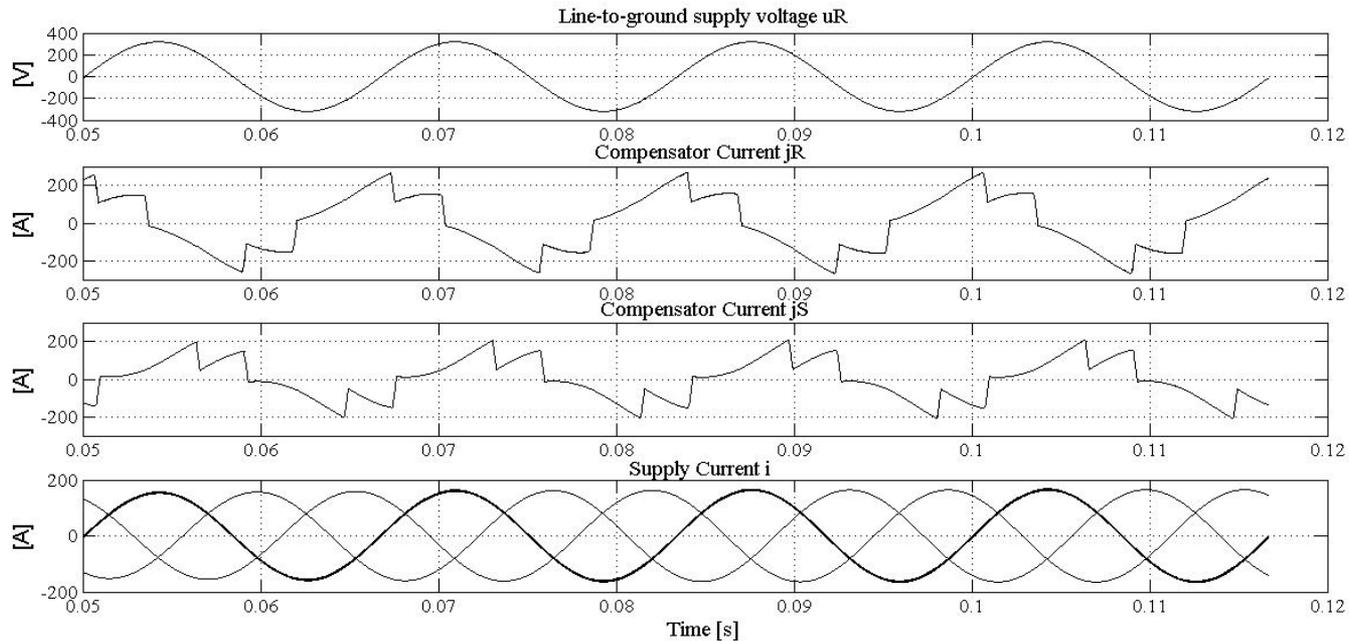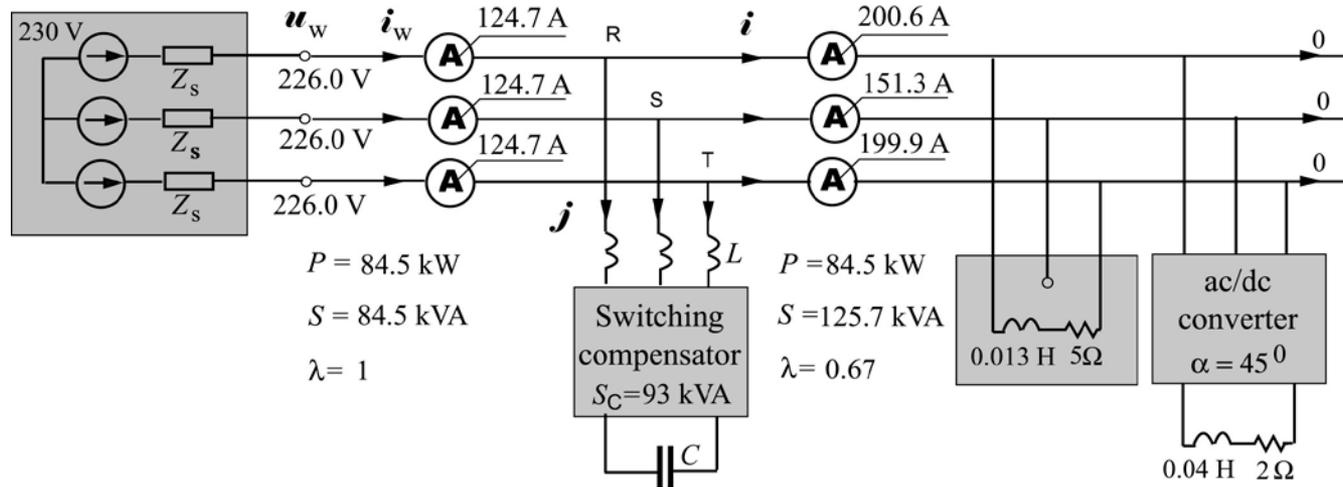Switching compensator with CPC - based control





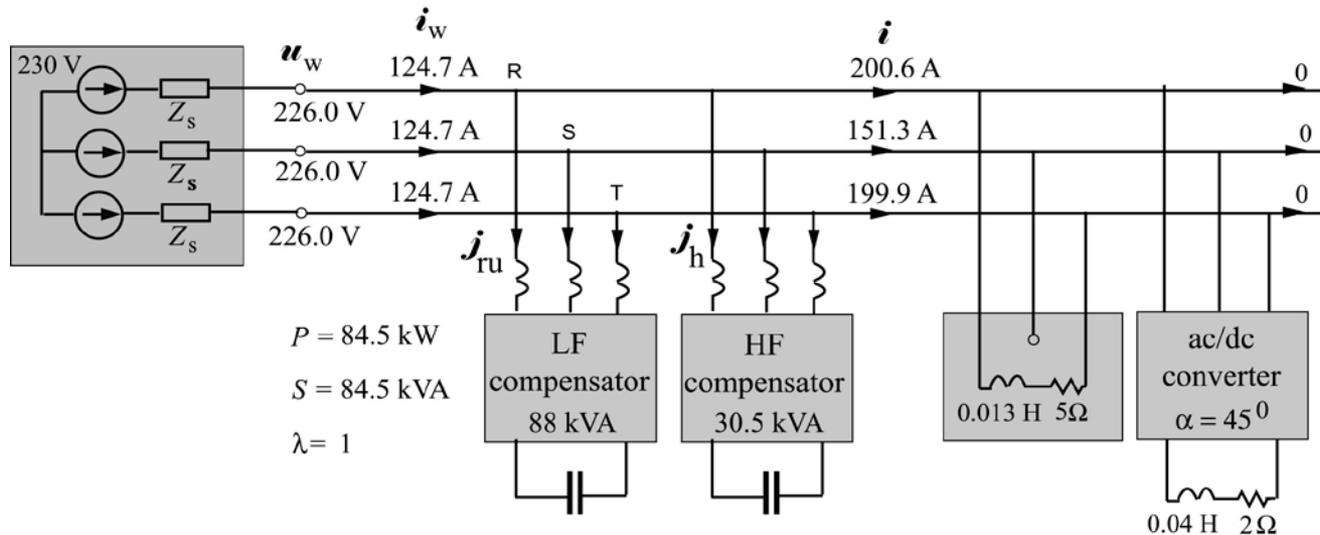Hybrid switching compensator with CPC-based control





Compensation of the generated current i_G requires fast switching inverter, but of low power

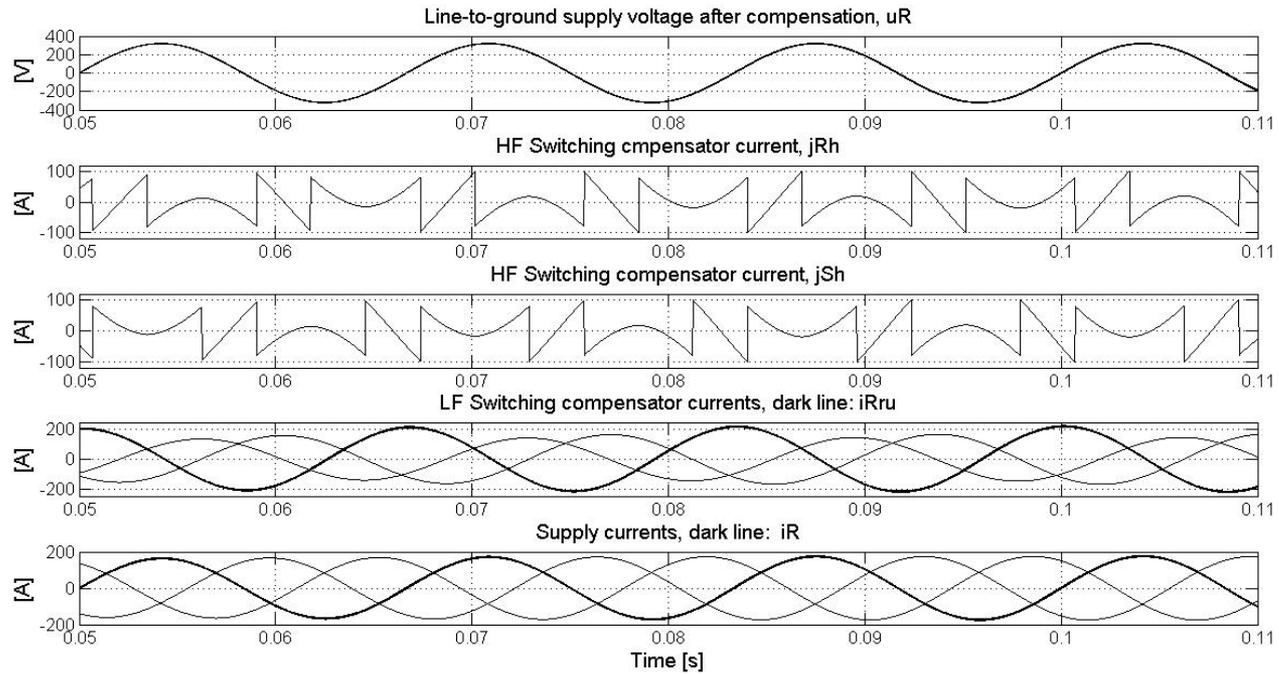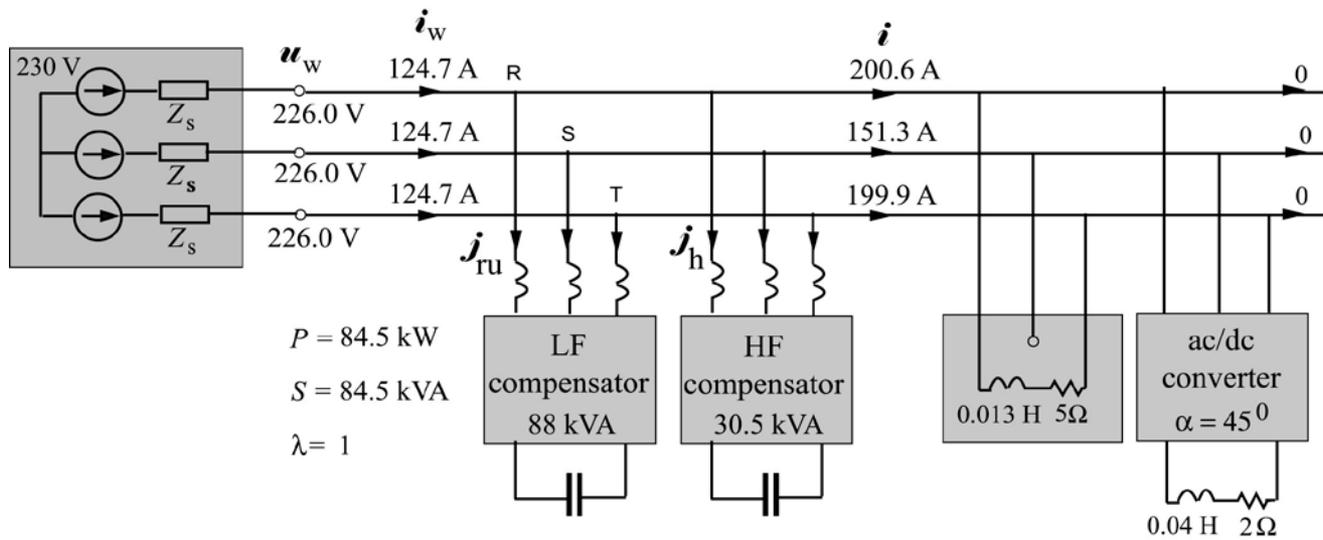
Compensation of the reactive and unbalanced currents i_r and i_u requires high power switching inverter, but the switching frequency can be low.



Loads with variable active power

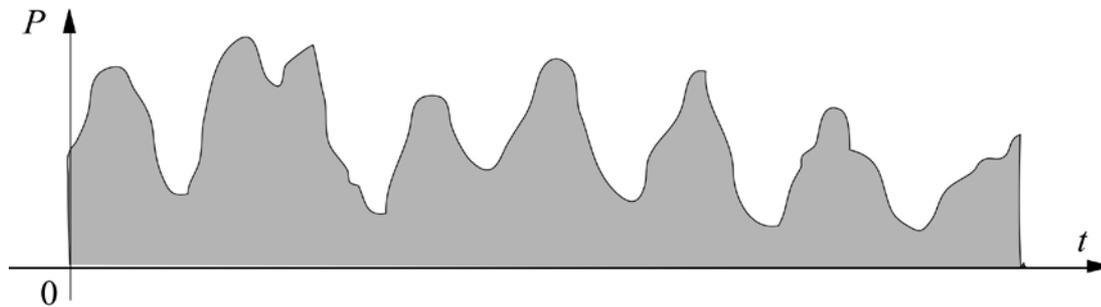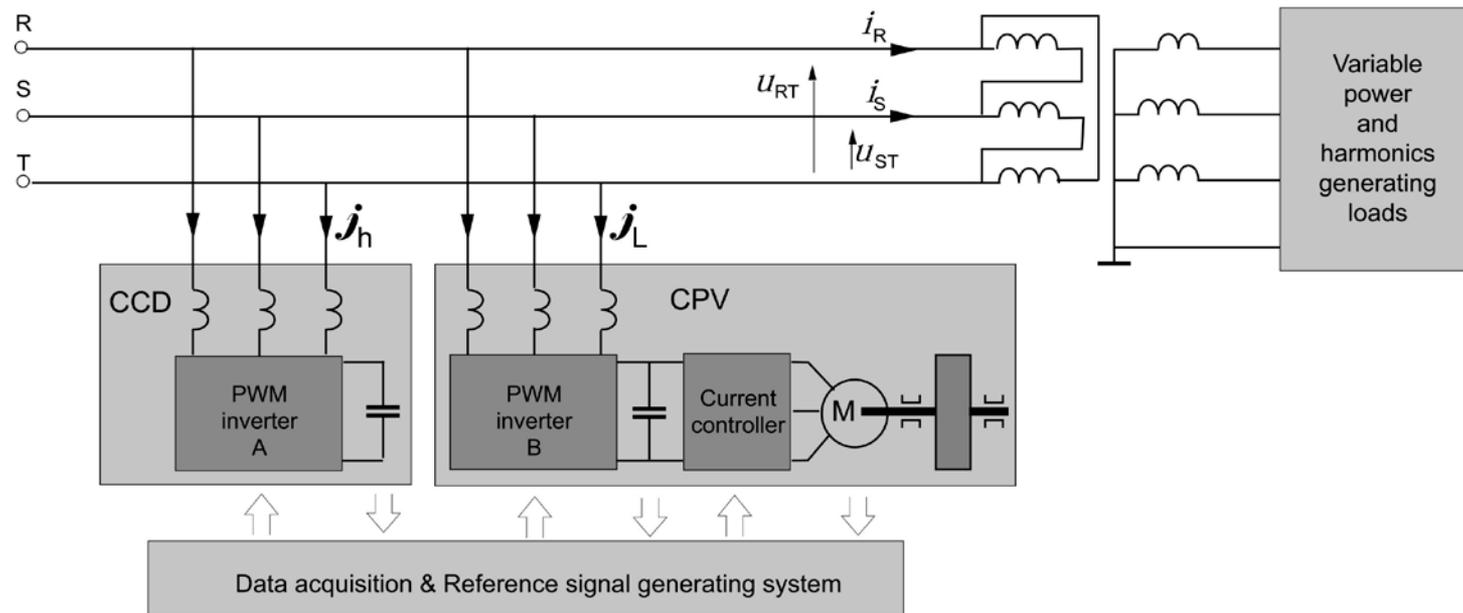



Loads with variable active power

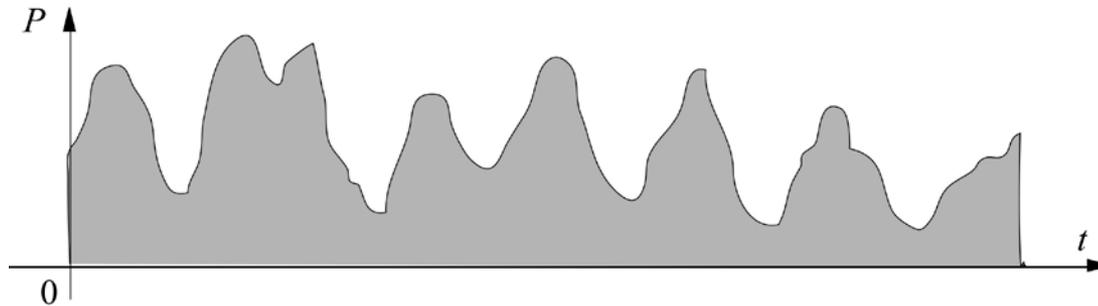

Compensation of a load with variable active power requires a compensator with a sufficient energy storage, but with low switching frequency

Compensation of the generated current does not require such energy storage, but higher switching frequency

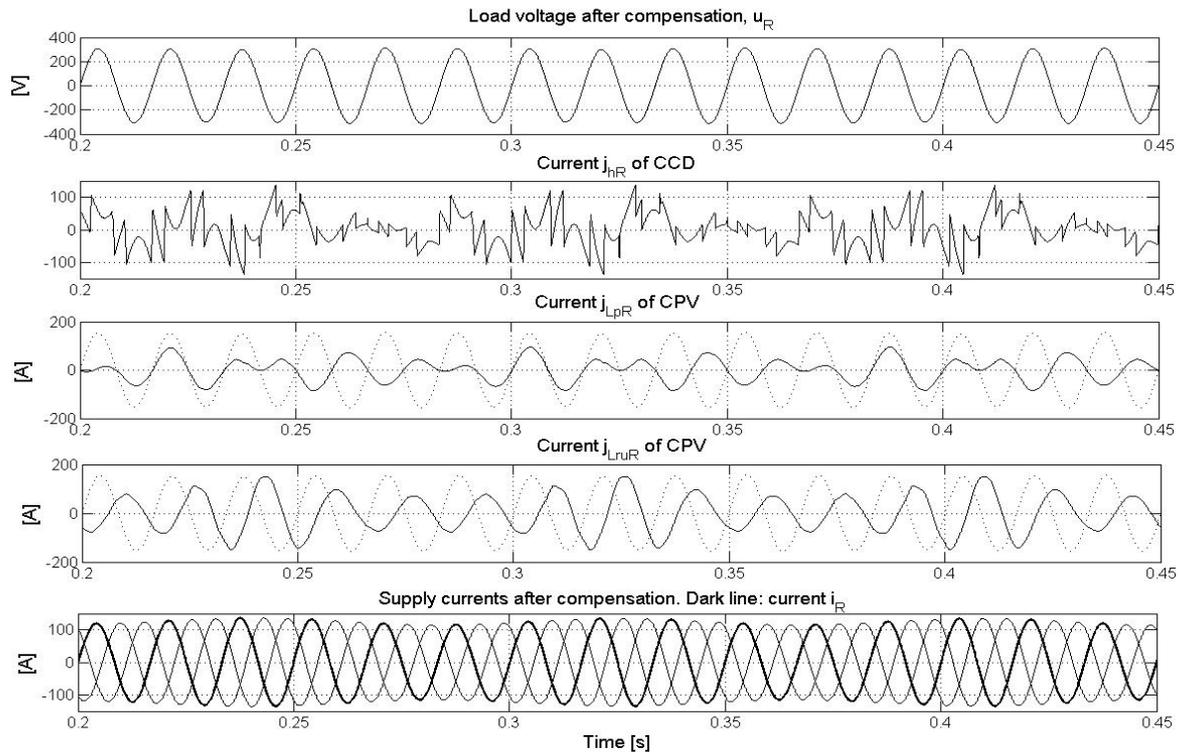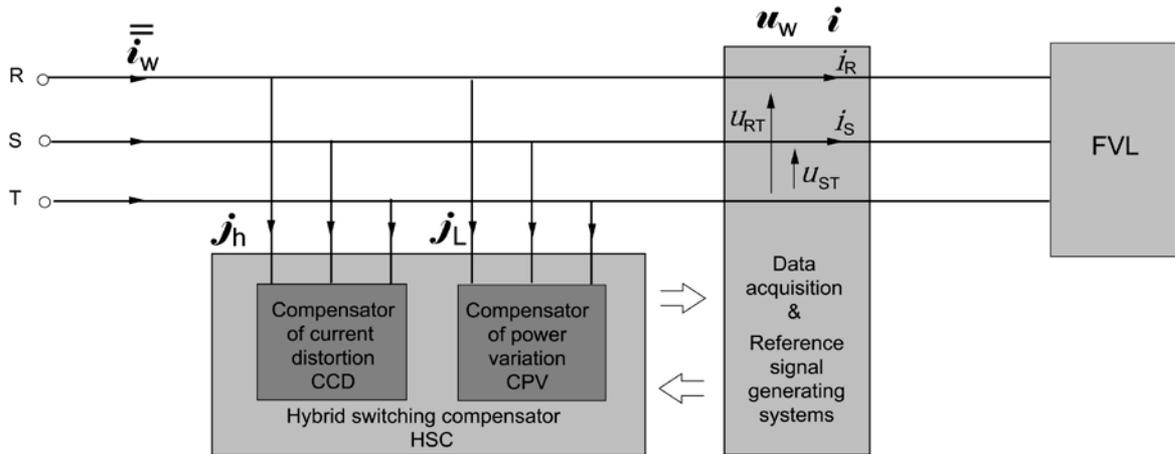Hybrid switching compensator with CPC-based control




Such compensation of individual current components
is not possible when a compensator
is controlled using
Instantaneous Reactive power p-q theory

$$\begin{bmatrix} u_\alpha \\ u_\beta \end{bmatrix} = \begin{bmatrix} \sqrt{3/2}, & 0 \\ 1/\sqrt{2}, & \sqrt{2} \end{bmatrix} \begin{bmatrix} u_R \\ u_S \end{bmatrix} \quad \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = \begin{bmatrix} \sqrt{3/2}, & 0 \\ 1/\sqrt{2}, & \sqrt{2} \end{bmatrix} \begin{bmatrix} i_R \\ i_S \end{bmatrix}$$

$$p = u_\alpha i_\alpha + u_\beta i_\beta$$

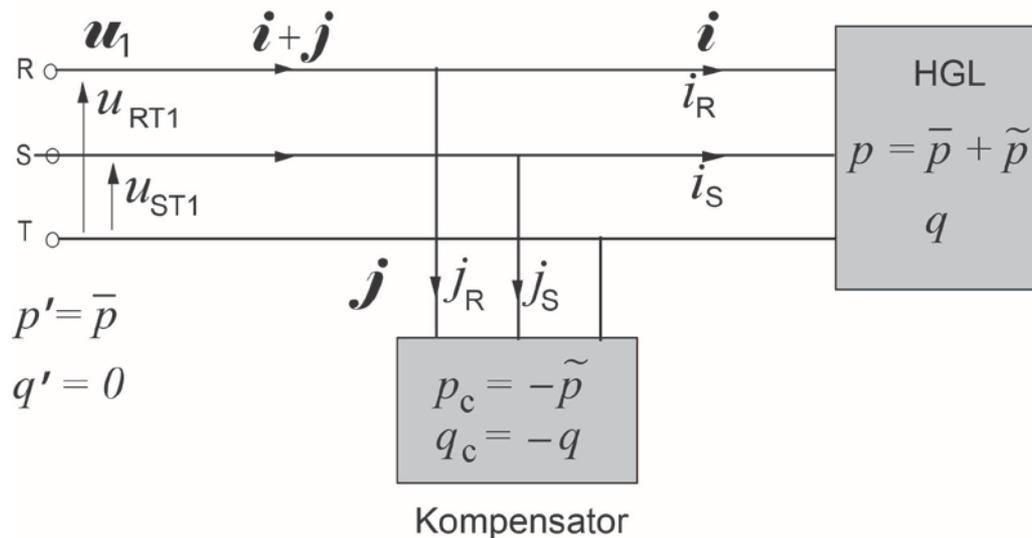
$$q = u_\alpha i_\beta - u_\beta i_\alpha$$



Moreover, IRP p-q Theory
erroneously interprets power phenomena in electrical circuits

$$u_R = \sqrt{2} U_1 \cos \omega_1 t,$$
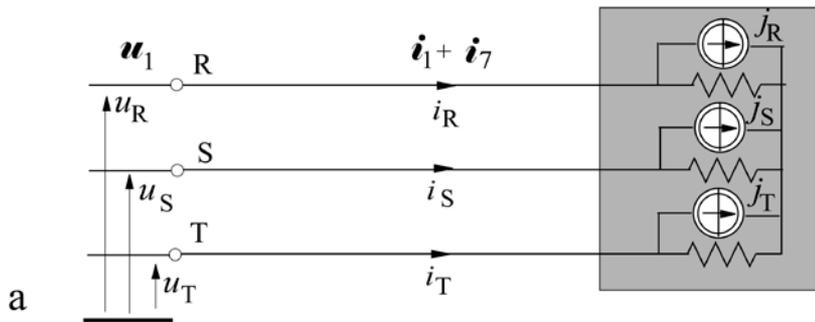
$$i_R = \sqrt{2} I_1 \cos \omega_1 t + \sqrt{2} I_7 \cos 7\omega_1 t$$




$$p = \bar{p} + \tilde{p} = 3U_1 I_1 + 3U_1 I_7 \cos 6\omega_1 t$$

$$q = 0$$

$$u_R = \sqrt{2} U_1 \cos \omega_1 t + \sqrt{2} U_7 \cos 7\omega_1 t$$

$$\mathbf{i} = \mathbf{G} \mathbf{u}$$

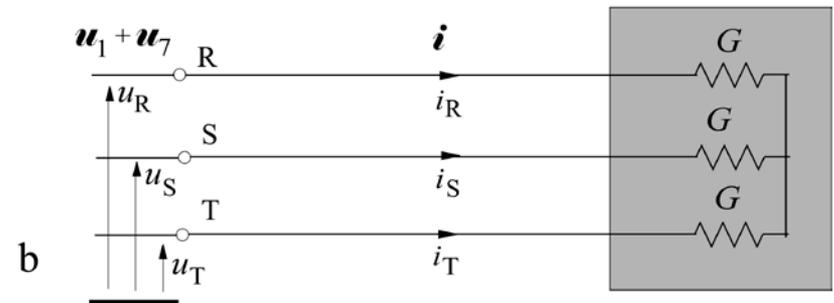

$$p = \bar{p} + \tilde{p} = P + 6GU_1 U_7 \cos 6\omega_1 t$$


$$q = 0$$

These two circuits,
substantially different with respect to properties and needed compensation,
are identical in terms of IRP p-q Theory

Moreover, the conclusion
that after ideal compensation the instantaneous active power p
should be constant ,
misinterprets power properties of electrical systems

The instantaneous active power p
of an ideal load
supplied with distorted voltage
or
asymmetrical voltage
IS
NOT CONSTANT

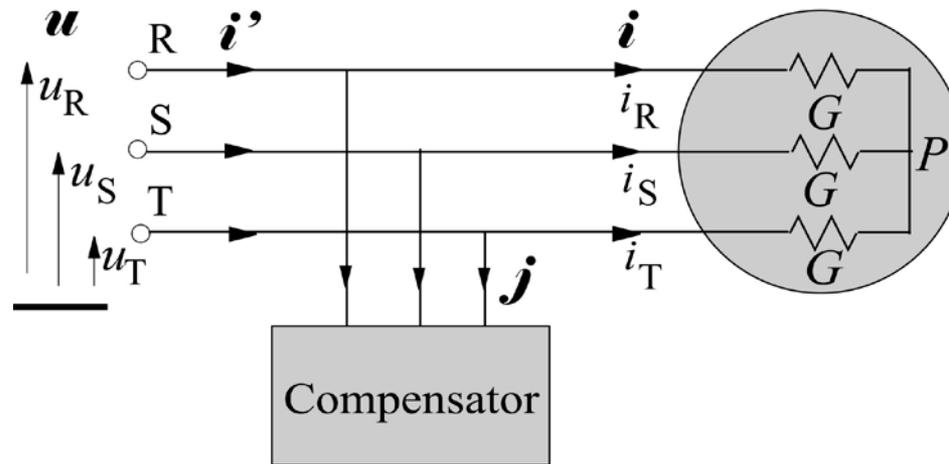
Let the load is an ideal resistive load supplied with nonsinusoidal voltage $\mathbf{u} = \mathbf{u}_1 + \mathbf{u}_5$



$$p = \bar{p} + \tilde{p} = P_1 + P_5 + 6GU_1U_5 \cos 6\omega_1 t$$

$$j_R = \frac{-2\sqrt{2}GU_1U_5 \cos 6\omega_1 t}{U_1^2 + U_5^2 + 2U_1U_5 \cos 6\omega_1 t} (U_1 \cos \omega_1 t + U_5 \cos 5\omega_1 t)$$

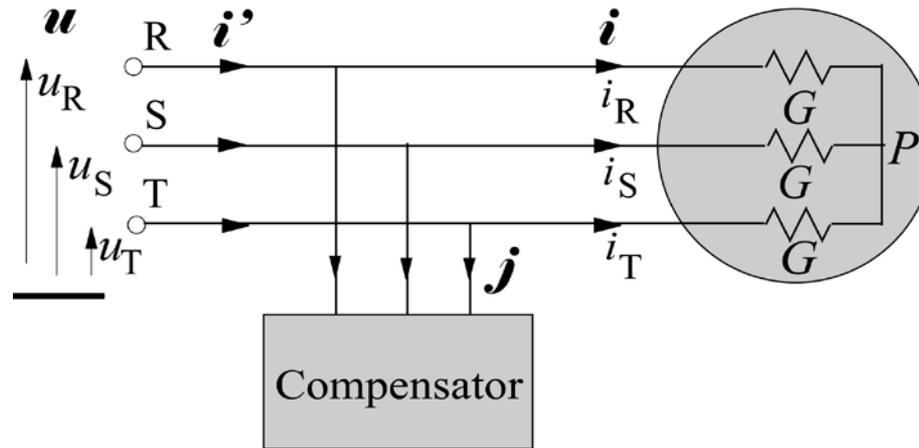Let the load is an ideal resistive load supplied with asymmetrical voltage $\mathbf{u} = \mathbf{u}^p + \mathbf{u}^n$



$$p = \bar{p} + \tilde{p} = P^p + P^n + 6GU^p U^n \cos 2\omega_1 t$$

$$j_R = \sqrt{\frac{2}{3}} j_\alpha = \frac{-2\sqrt{2} G(U^p + U^n)U^p U^n \cos \omega_1 t \cos 2\omega_1 t}{U^{p2} + U^{n2} + 2U^p U^n \cos 2\omega_1 t}$$

L.S. Czarnecki, "Effect of supply voltage asymmetry on IRP p-q - based switching compensator control," *IET Proc. on Power Electronics*, 2010, Vol. 3, No. 1

Development
of the Currents' Physical Components (CPC) – based Power Theory


was strongly correlated with evaluation of results

of other approaches
to this Theory development

**Short overview of results of various approaches
to power theory development**

Currents' Physical Components (CPC)

Power Theory

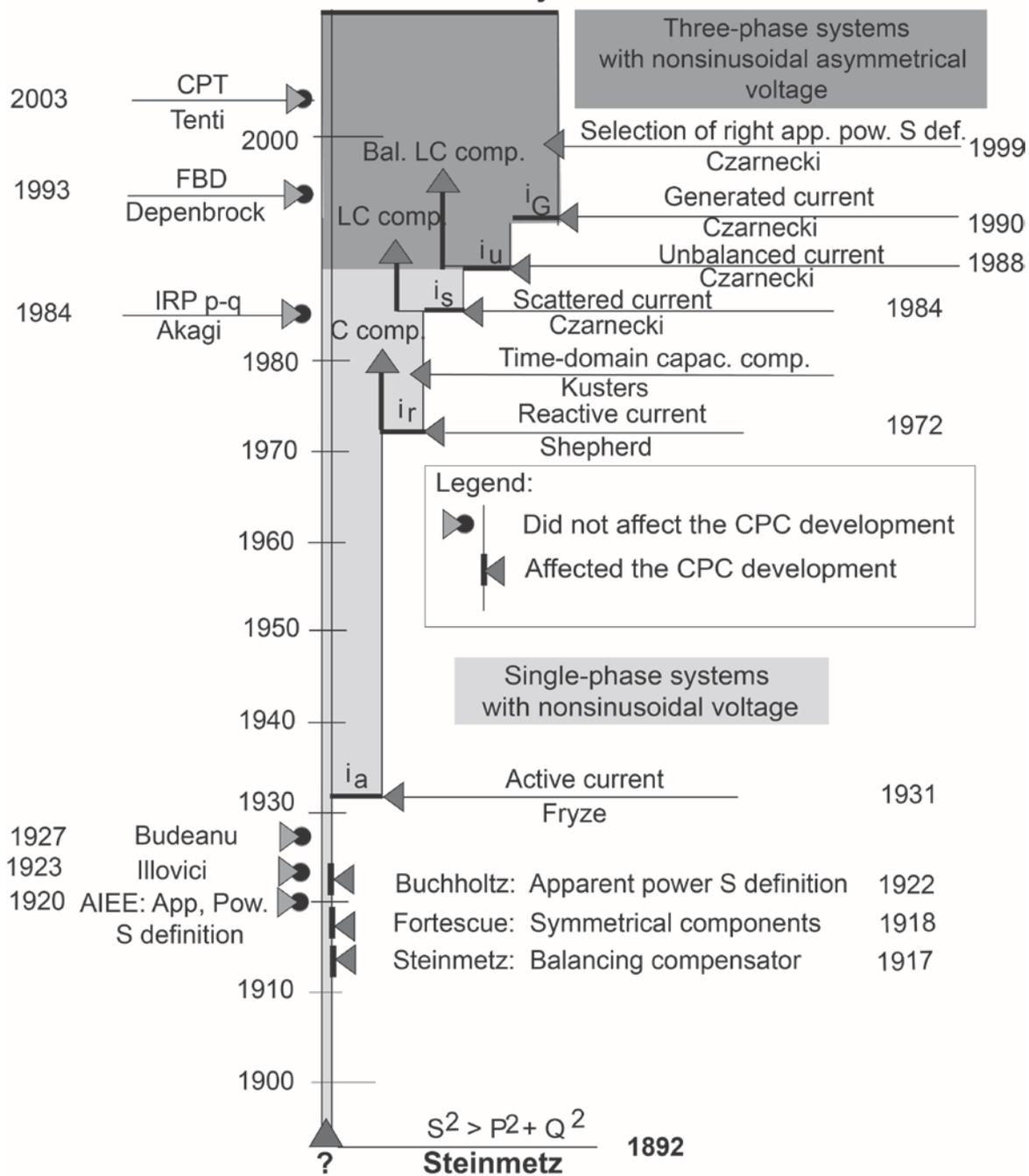

Budeanu (1927) Power Theory: (In the frequency-domain)

Endorsed by the IEEE Standard Dictionary of Electrical and Electronics Terms in 1992
and German Standards DIN in 1972

- Reactive and distortion powers Q and D are not associated with any power phenomena
- It does not provide fundamentals for compensation

L.S. Czarnecki, "What is wrong with the Budeanu concept of reactive and distortion powers and why it should be abandoned," *IEEE Trans. Instr. Meas.*, Vol. IM-36, No. 3, pp. 834-837, Sept. 1987.

L.S. Czarnecki, "Budeanu and Fryze: Two frameworks for interpreting power properties of circuits with nonsinusoidal voltages and currents," *Archiv fur Elektrotechnik*, (81), N. 2, pp. 5-15, 1997.

Fryze (1931) Power Theory (In the time-domain)

Endorsed by German Standards DIN in 1972

- It introduced the concept of the active current
- It introduced the concept of the current orthogonal decomposition
- It does not provide physical interpretation of power phenomena
- It does not provide fundamentals for reactive compensation

L.S. Czarnecki, “Budeanu and Fryze: **Two frameworks for interpreting power properties of circuits with nonsinusoidal voltages and currents,**”
Archiv fur Elektrotechnik, (81), N. 2, pp. 5-15, 1997.

Shepherd and Zakikhani (1972) Power Theory (In the frequency-domain)

- It introduced the concept of the reactive current
- It solved the problem of optimal capacitive compensation at nonsinusoidal supply voltage

L.S. Czarnecki, "Comments on reactive powers as defined by Kusters and Moore for nonsinusoidal systems," *Rozprawy Elektrotechniczne*, Tom XXX, Z. 3-4, pp. 1089-1099, 1984.

Kusters and Moore (1980) power theory (In the time-domain)

Endorsed by the International Electrotechnical Commission in 1980

- It solved the problem of optimal capacitive compensation at nonsinusoidal supply voltage in time-domain

L.S. Czarnecki, "Additional discussion to "Reactive power under nonsinusoidal conditions," *IEEE Trans. on Power and Systems*, Vol. PAS-102, No. 4, April 1983.

L.S. Czarnecki, "Comments on reactive powers as defined by Kusters and Moore for nonsinusoidal systems," *Rozprawy Elektrotechniczne*, Tom XXX, Z. 3-4, pp. 1089-1099, 1984.

**Nabae and Akagi (1984):
Instantaneous Reactive Power p-q Theory
(in the time-domain)**

- It solved the problem of compensation in three-phase of unbalanced, harmonics generating loads supplied with sinusoidal and symmetrical supply voltage
 - It does not describe power properties of systems with nonsinusoidal supply voltage
- It misinterpretes power phenomena in three-phase systems

L.S. Czarnecki, "On some misinterpretations of the Instantaneous Reactive Power p-q Theory," *IEEE Trans. on Power Electronics*, Vol. 19, No.3, pp. 828-836, 2004.

L.S. Czarnecki, "Comparison of the Instantaneous Reactive Power, p-q, Theory with Theory of Current's Physical Components," *Archiv fur Elektrotechnik*, Vol. 85, No. 1, Feb. 2004, pp. 21-28.

L.S. Czarnecki, "Effect of supply voltage harmonics on IRP-based switching compensator control," *IEEE Trans. on Power Electronics*, Vol. 24, No. 2, Feb. 2009. pp. 483-488.

L.S. Czarnecki, "Effect of supply voltage asymmetry on IRP p-q - based switching compensator control," *IET Proc. on Power Electronics*, 2010, Vol. 3, No. 1, pp. 11-17.

L.S. Czarnecki, "Constraints of the Instantaneous Reactive Power p-q Theory", *IET Power Electronics*, Vol. 7, No. 9, pp.2201-2208, 2014.

Depenbrock (1993) the FBD Method (In the time-domain)

- It generalizes Fryze's power theory to three-phase systems
 - It correctly defines the apparent power S
 - It does not provide interpretation of power phenomena
- It does not provide fundamentals for reactive compensation

Tenti (2003): The Conservative Power Theory (CPT),
formulated by in the time-domain

- It misinterpretes power phenomena
- It does not provide right fundamentals for compensation

L.S. Czarnecki: **Critical comments on the Conservative Power Theory (CPT)**, *Przegląd Elektrotechniczny (Proc. of Electrical Engineering)*, R3, No. 1, pp. 268-274, 2017.

L.S.Czarnecki: **What is Wrong with the Conservative Power Theory (CPT)**, *Int. Conference on Applied and Theoretical Electrical Eng. (ICATE) Romania*, 2016

Why the apparent power S is higher than the active power P ?

How the difference between S and P can be reduced ?

Key Note

at

25th Iranian Conference on Electrical Engineering (ICEE 2017)
Tehran, Iran, May 2017

**Currents' Physical Components (CPC) – based power theory
of electrical systems
with nonsinusoidal and asymmetrical voltages and currents: –
– present state and the future**

Leszek S. Czarnecki, IEEE Life Fellow

Titled Professor of Technological Sciences of Poland
Distinguished Professor at School of Electrical Engineering
Louisiana State University, USA

Internet Page: www.lsczar.info

To keep a healthy distance to what I told,
a power system engineer
after such a presentation told:

*„It does not matter that
the apparent power S is higher than the active power P .
Eventually
customers pay for everything”*

Thanks for your attantion!!

با تشکر از توجه شما